
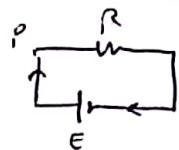


Alternating Current

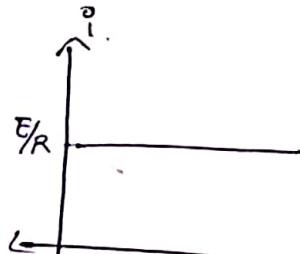

$$i = \frac{E}{R} = \text{constant}$$



Direct current



AC Source





$$e = B\omega\pi R^2 \sin\omega t$$


$$e = e_0 \sin\omega t$$

$$i = \frac{e_0}{R} \sin\omega t$$

$$i = i_0 \sin\omega t$$

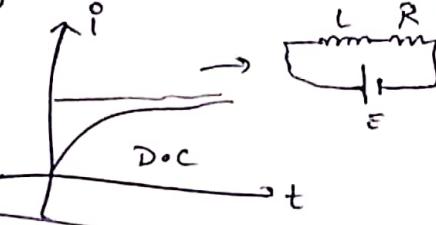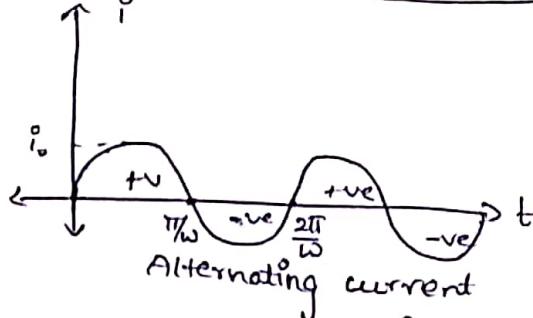



DC Source

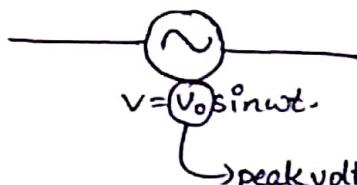

$$v = V_0 \sin\omega t$$

peak voltage.
(max voltage)

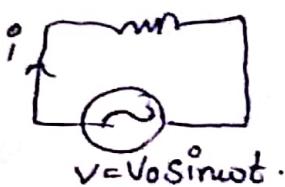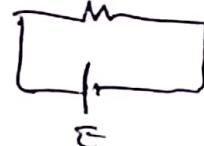ω - angular frequency
frequency of source = $\frac{\omega}{2\pi}$



$$v = V_0 \sin\omega t$$


Current in the circuit

$$i = \frac{v}{R} = \frac{V_0 \sin\omega t}{R}$$

$$i = \left(\frac{V_0}{R}\right) \sin\omega t$$

$$i = i_0 \sin \omega t$$

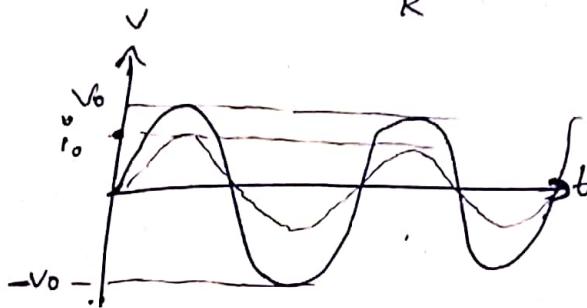peak current = $\frac{\text{peak voltage}}{R}$



* In the resistor, voltage and current will be in same phase.

Measurement of A.C Values.

$$i = i_0 \sin \omega t$$

$$\langle \sin^2 \omega t \rangle = \langle \cos^2 \omega t \rangle = \frac{1}{2}$$

Average value :-

$$\langle \sin \omega t \rangle = \langle \cos \omega t \rangle = 0$$

If AC is given by $i = i_0 \sin \omega t$

Average value of current in one time period (T)

$$\langle i \rangle = \frac{\int i dt}{\int dt} = \frac{\int_0^T i_0 \sin \omega t dt}{\int_0^T dt}$$

$$= i_0 \left(\frac{-\cos \omega t}{\omega} \right)_0^T$$

$$\frac{1 - \cos \omega T}{2}$$

$$= 1 -$$

$$\langle i \rangle = \frac{i_0}{T} \left(\frac{\cos 0 - \cos \omega T}{\omega} \right)$$

$$\langle i \rangle = \frac{i_0}{T} \left(\frac{-1 + 1}{\omega} \right) = 0$$

$$\langle i \rangle = 0$$

Q) Find the average value of current. $i = i_0 \sin^2(\omega t)$

Ans

$$\langle i \rangle = \frac{i_0}{2} \int_0^T 1 - \cos(2\omega t) dt$$

$$\langle i \rangle = \frac{i_0}{2} \left(t - \frac{\sin 2\omega t}{2\omega} \right)_0^T$$

$$\langle i \rangle = \frac{i_0}{2} \left(\frac{T}{2} \right)$$

$$\langle i \rangle = \frac{i_0}{2}$$

If a voltage is given by $V = 3 + 4\sin^2\omega t$. Find the average value of voltage.

$$\langle V \rangle = \langle 3 \rangle + 4 \langle \sin^2\omega t \rangle \\ = (3) + 4 \times \frac{1}{2} \\ \langle V \rangle = 5$$

$$i_{rms}^2 =$$

RMS

Root mean square

If current in the element is $i = i_0 \sin\omega t$.

$$i_{avg} = 0$$


$$i^2 = (i_0 \sin\omega t)^2 \\ i_{rms}^2 = \sqrt{\langle i^2 \rangle}$$

$$P = \sqrt{i_0^2 \sin^2\omega t}$$

$$i^2 = \sqrt{i_0^2 \langle \sin^2\omega t \rangle}$$

$$i = \frac{i_0}{\sqrt{2}}$$

$$i_{rms} = \frac{i_{peak}}{\sqrt{2}}$$

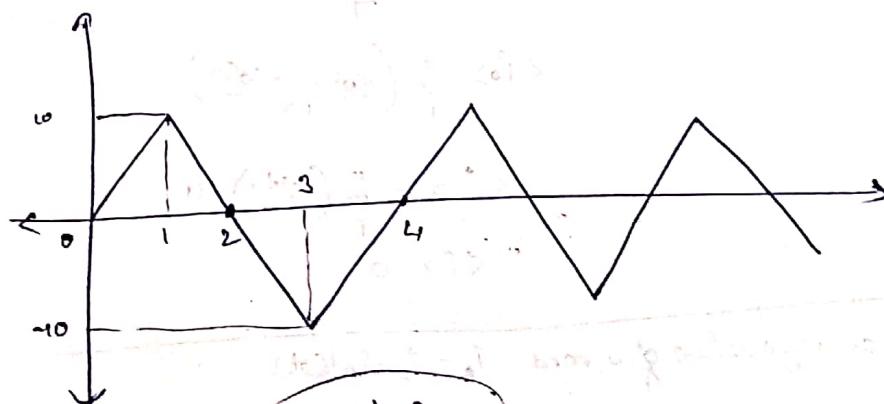

$$i = 10 \sin(\omega t) \quad T = 4 \text{ sec}$$

$$\sin^{-1}\omega t$$

$$\frac{10}{\sqrt{2}}$$

$$\frac{1}{\sqrt{1 - x^2}}$$

$$x \sin^{-1} x$$

$$\int \sin^{-1} x \, dx$$

$$\sin^{-1} x \cdot x - \int \frac{x}{\sqrt{1-x^2}} \, dx$$

$$[x \sin^{-1} x + \sqrt{1-x^2}]$$

$$6 \text{ stars} \\ (-100%)$$



$$i_{rms}^2 = \frac{\int i^2 dt}{\int dt} = \frac{\int i^2 dt}{T} = \frac{\int i^2 dt}{T} + \frac{\int i^2 dt}{T}$$

$$i_{rms} = \sqrt{\frac{\int (at)^2 dt + \int (a\cos\omega t)^2 dt + \int (a\sin\omega t)^2 dt}{T}}$$

$$i_{rms} = 5 \text{ amp.}$$

approx
val

AC Measuring Instruments

hot wire ammeter / hot wire voltmeter


A hot wire ammeter (or) voltmeter will always show a thereading
Circ of rms value.

- a) If current in the element is $i = 3+4\sin\omega t$, find the reading by hot wire ammeters?

$$\begin{aligned} i_{rms} &= \sqrt{\langle i^2 \rangle_{avg}} = \sqrt{(3+4\sin\omega t)^2} \\ &= \sqrt{9+16\sin^2\omega t + 24\sin\omega t} \\ &= \sqrt{9+8} \\ i_{rms} &= \sqrt{17} \end{aligned}$$

Ques) The reading of voltmeter = ?
(?)

Behaviour of Resistance with AC Source.

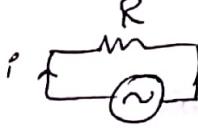


$$i = \left(\frac{V_0}{R}\right) \sin \omega t$$

$$i = i_0 \sin \omega t$$

Current & Voltage are in same phase in resistors.

Phasors-

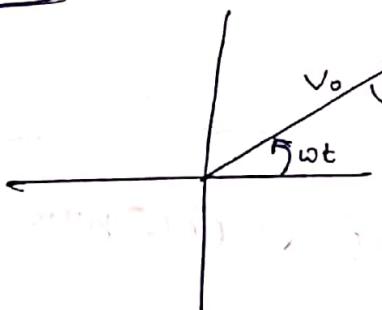


$v = v_0 \sin(\omega t)$ with an angle ωt with horizontal line:

length of magnitude v_0

⇒ Phasors rotates about origin

Behaviour of Capacitor with AC source

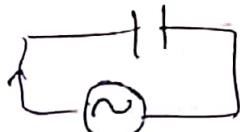

$$v = v_0 \sin \omega t$$

$$\text{Current in circuit} = i = C v_0 \omega \cos \omega t$$

$$i = i_0 \cos \omega t$$

$$i = i_0 (\sin(\omega t + \pi/2))$$

Current and Voltage will differ by phase angle $\pi/2$ in capacitor

Current leads voltage by $\pi/2$ phase.


$$i_0 = C v_0 \omega$$

$$i = \frac{v_0}{(1/X_C)}$$

$\frac{1}{\omega X_C}$ = Reactance of capacitor to AC current (X_C)


$$X_C = \frac{1}{\omega C}$$

$$X_C = \frac{1}{2\pi f C}$$

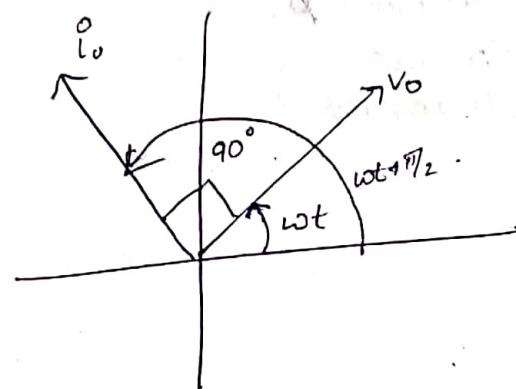

Cur leads in Capa

Behaviour of Inductor with AC Source

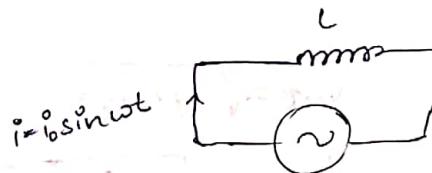


$$P.d. \text{ across inductor} = L \frac{di}{dt}$$

$$v_o = L i_0 \omega \cos \omega t$$

$$v = v_0 \cos \omega t$$

$$v = v_0 \sin(\omega t + \pi/2)$$

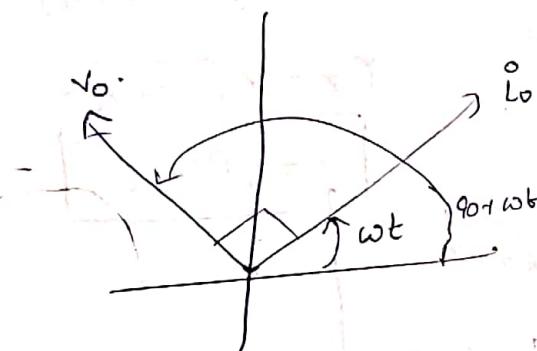Voltage leads current in ~~the~~ inductor by phase angle $\pi/2$.



$$v_o = i_0 (\omega L)$$

Reactance of Inductor $X_L = \omega L = 2\pi f L$

Past Knowledge

$$y_1 = A_1 \sin(\omega t)$$

$$y_2 = A_2 \sin(\omega t + \phi)$$

$$\therefore y = A \sin(\omega t + \theta)$$


A

$$A = \sqrt{A_1^2 + A_2^2 + 2A_1 A_2 \cos \phi}$$

$$\theta = \tan^{-1} \left(\frac{A_2 \sin \phi}{A_1 + A_2 \cos \phi} \right)$$


LR

(R Circuit) in AC

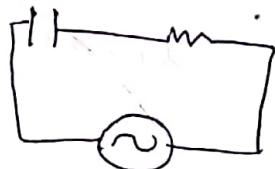

$$i_1 = i_2 \sin \omega t$$

$$i_2 = i_2' \sin(\omega t + \pi/2)$$

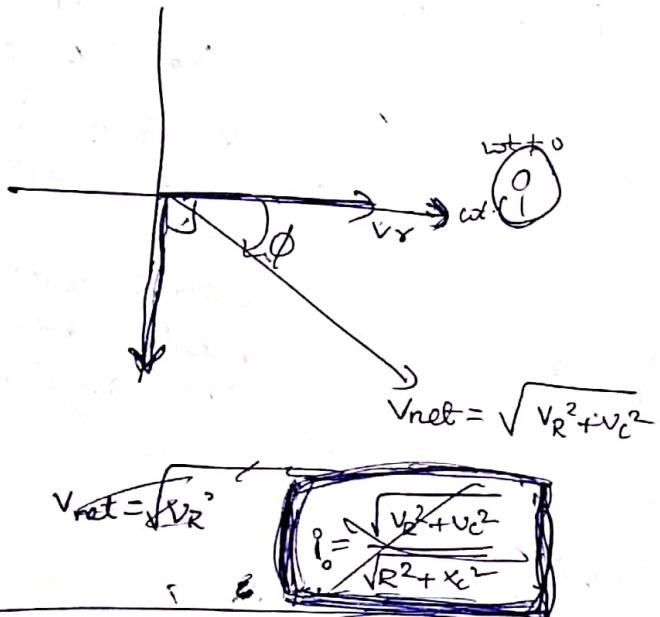

$$V_{net} = \sqrt{V_R^2 + V_C^2}$$

$$i_Z = \sqrt{(iR)^2 + (iX_C)^2}$$

$$i_Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{R^2 + X_C^2}$$

Impedance of circuit.

$$\tan \phi = \frac{V_C}{V_R} = \frac{i X_C}{i R}$$



$$\tan \phi = \left(\frac{X_C}{R} \right)$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right)$$

; Current in circuit $\Rightarrow i = i_0 \sin(\omega t + \phi)$

$$i_0 = \frac{V_0}{\sqrt{R^2 + X_C^2}}$$

LRC circuit in AC

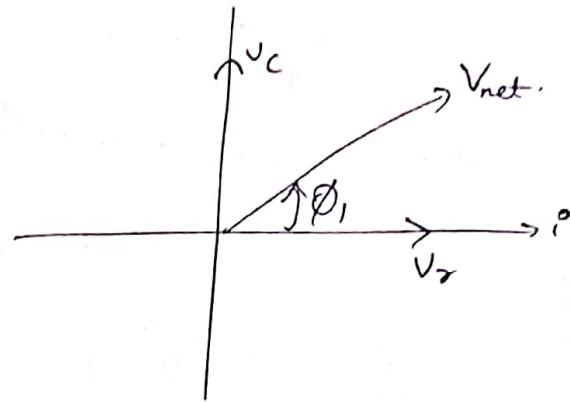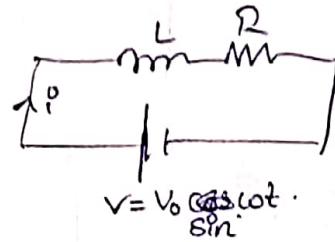

V_{net}

$$i = i_0 \sin(\omega t - \phi)$$

V_{net}

$$i_0 = \frac{V_0}{\sqrt{R^2 + X_L^2}}$$

$$V_{net} = \sqrt{V_C^2 + V_R^2}$$

$$iZ = \sqrt{(X_L i)^2 + (iR)^2}$$


$$iZ = i \sqrt{(X_L)^2 + R^2}$$

$$Z = \sqrt{(X_L)^2 + R^2}$$


$$\tan \theta = \frac{V_C}{V_R}$$

$$\theta = \tan^{-1} \left(\frac{X_L}{R} \right)$$

LCR series circuit

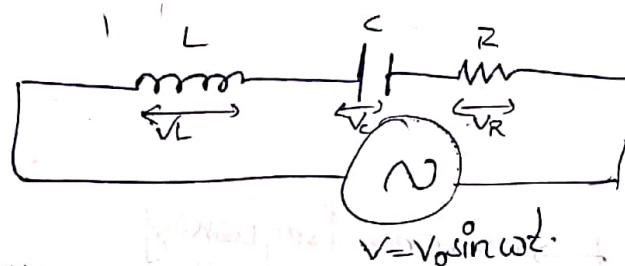


difference lesser
the higher

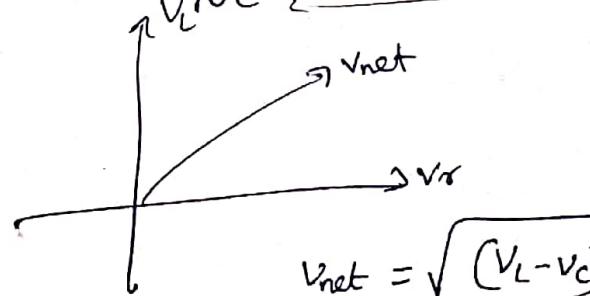

$$V_{net} = \sqrt{(V_L - V_C)^2 + V_R^2}$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

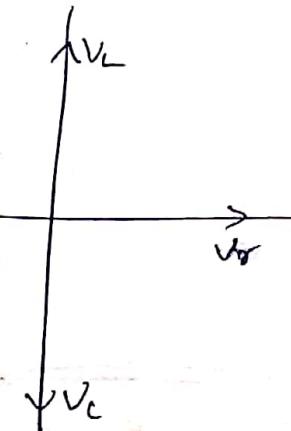


$$\tan \phi = \frac{V_L - V_C}{V_R}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

• If voltage leads current by ϕ

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$


Circuit behaves as inductive.

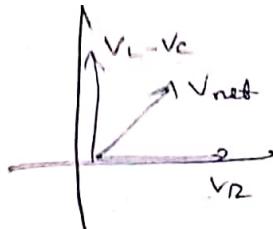

• If $X_C > X_L$, current leads voltage by ϕ

$$\phi = \tan^{-1}\left(\frac{X_C - X_L}{R}\right)$$

Circuit acts as capacitive.

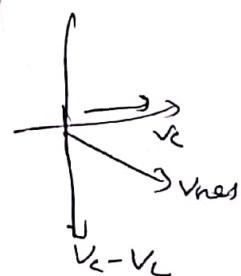

• If $X_L = X_C$, $V_L = V_C$

$$Z_{\text{min}} = R$$

Current is maximum

Resonable condition.

Circuit nature is resistive.

At resonance

$$X_C = X_L$$

$$\frac{1}{\omega C} = \omega L$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$\boxed{f = \frac{1}{2\pi\sqrt{LC}}} \rightarrow \text{resonance frequency.}$$

Power in AC

Suppose current in circuit is $i = I_0 \sin \omega t$
 $v = V_0 \sin(\omega t + \phi)$

Instantaneous power delivered is $P_{inst} = v i$
 $P_{inst} = V_0 I_0 \sin \omega t \sin(\omega t + \phi)$

Average power in one time period is

$$\langle P \rangle = \frac{\int_0^T P dt}{\int_0^T dt}$$

$$\langle P \rangle = \langle V_0 I_0 \sin(\omega t) \sin(\omega t + \phi) \rangle$$

$$= V_0 I_0 \langle \sin \omega t \sin(\omega t + \phi) \rangle$$

$$= V_0 I_0 \langle \sin(\omega t) [\sin \omega t \cos \phi + \cos \omega t \sin \phi] \rangle$$

$$= V_0 I_0 [\langle \sin^2(\omega t) \cos \phi \rangle + \langle \sin \omega t \cos \omega t \sin \phi \rangle]$$


$$= V_0 I_0 \left[\omega \sin \phi \times \frac{1}{2} + \sin \phi \times 0 \right]$$

$$\langle P \rangle = V_0 I_0 \cos \phi$$

$$P_{avg} = \left(\frac{V_0}{\sqrt{2}} \right) \left(\frac{I_0}{\sqrt{2}} \right) \cos \phi$$

$$P_{avg} = V_{rms} \cdot I_{rms} \cos \phi$$

$\cos \phi \rightarrow$ power factor

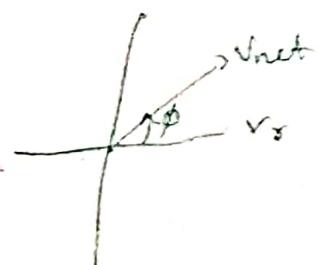

$$\cos \phi = \frac{V_R}{V_{net}} = \frac{I_0 R}{I_0 Z} = \frac{R}{Z}$$

$$P_{avg} = V_{rms} V_{rms} \cdot \frac{R}{Z} = \left(\frac{V_{rms}}{\sqrt{2}}\right)^2 \frac{R}{Z}$$

$$\boxed{P_{avg} = \left(\frac{V_{rms}}{\sqrt{2}}\right)^2 R}$$

$$P_{avg} = V_{rms} I_{rms} \cos \phi$$

$$= (I_{rms} Z) (I_{rms}) R$$

$$\boxed{P_{avg} = (I_{rms})^2 R}$$


Note:-

In LCR series circuit, at resonance

$$\text{Power factor} = \cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X^2}}$$

$$\cos \phi = 1 \\ \phi = 0^\circ$$

(Q)

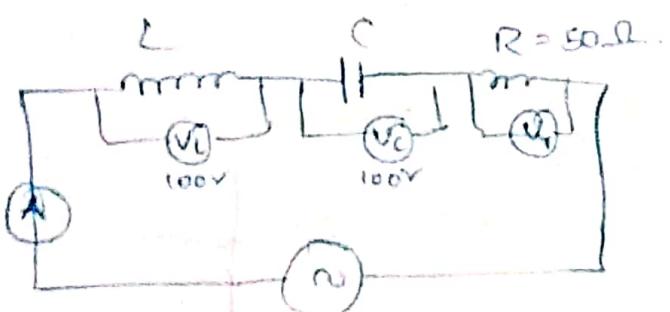

$$V_{rms} = 100V$$


$$\boxed{V_r = 200 \text{ Volts}}$$

$$2\pi f = 50$$

$$w = 100\pi$$

$$I = 4 \text{ Amp}$$

a)

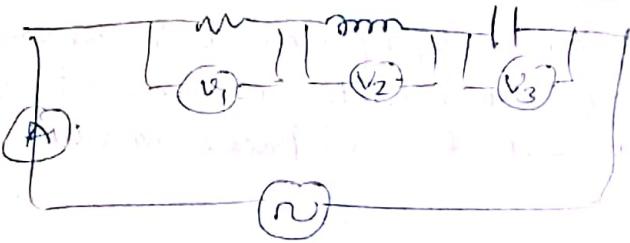

$$V_{\text{net}}$$

$$E = E_0 \sin \omega t$$

$$V_1 = 100V$$

$$V_2 = 125^\circ V$$

$$V_3 = 150$$

$$28^2 + 100^2$$

$$\sqrt{625 + 10000} = \sqrt{1625}$$

$$\therefore V_{\text{net}} = \sqrt{1625}$$

Find (a) Net impedance

(b) Power factor.


$$\cos \phi = \frac{R}{Z} = \frac{28}{\sqrt{17 \times 5}} = \frac{4}{\sqrt{17}}$$

$$Z = \frac{V_{\text{net}}}{I} = \frac{\sqrt{1625}}{5} = \frac{\sqrt{1625}}{25} = \frac{1625}{25} = \sqrt{650}$$

$$= \sqrt{425}$$

$$\boxed{Z = 25 \sqrt{17}}$$

b)

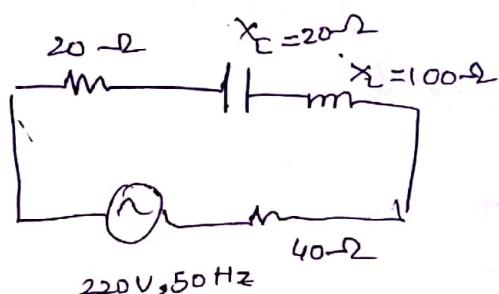

$$\frac{1}{\omega C} = 20$$

$$\therefore \omega L = 100$$

$$Z = \sqrt{(100-20)^2 + 60^2}$$

$$= \sqrt{80^2 + 60^2} = 100\Omega$$

$$\cos \phi = \frac{R}{Z} = \frac{20}{100} = 0.2$$

$$\frac{60}{6400 \times 3600}$$

$$10000$$

$$\frac{3}{5} \frac{60}{60}$$

$$60 \angle 0^\circ$$

$$-NH_2 \quad N_2$$

Q)

In a LCR series circuit 100Ω is connected to AC source of $200V$, $\omega = 300 \text{ rad/s}$. When only capacitance is removed current lags behind voltage by 60° . If only inductor is removed current leads voltage by 60° . Find current and Power in LCR circuit.


Note

~~Ans:~~

$$R = 100$$

$$V_0 = 200$$


$$\omega = 300 \text{ rad/s.}$$

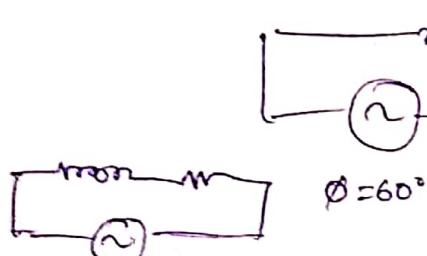

$$\phi = 60^\circ$$

$$\tan \phi = \frac{x_L}{R}$$

$$x_L = \sqrt{3} R$$

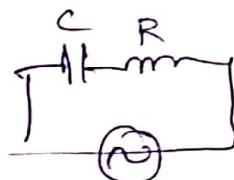

$$\tan \phi = \frac{x_C}{R}$$

$$x_C = \sqrt{3} R$$

$$\textcircled{*} Z = R$$

$$I_{\text{rms}} = \frac{200}{100} = 2 \text{ amp.}$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos \phi$$

$$= 200 \times 2$$

$$P = 400 \text{ Watts}$$

Q) In LCR series circuit $R = 100\Omega$ are connected in series with source of $20V$ & 750Hz . Find the time in which $L = 180 \times 10^{-3} \text{ H}$ $C = 10 \times 10^{-6} \text{ F}$.

Resistance having $\omega =$ thermal capacity 25J/S° will get heated by 10° .

$$x_L = \omega L = 180 \times 10^{-3} \times 750 \quad x_C = \frac{1}{\omega C} = \frac{1}{10 \times 10^{-6} \times 750}$$

$$= \frac{18 \times 75}{10^2} \times$$

$$P = 20 \quad x_L = 22.5 \Omega$$

$$V_{\text{rms}} = 400 \sqrt{3}$$

$$x_C = \frac{10^4}{75}$$

$$= \frac{100 \times 10^2}{75 \times 3}$$

$$x_C = \frac{100}{22 \times 3 \times 3} = \frac{133.3}{21 \times 3}$$


$$= 6480 \Omega$$

$$\langle P \rangle = \frac{20 \times 20 \times 100}{100^2 + (x_L - x_C)^2} \quad (x_L - x_C)^2$$


heat generated = $\langle P \rangle t$.

$$20 = \langle P \rangle t \quad t = \frac{20}{\langle P \rangle} \approx 45 \text{ sec}$$

Note for In LCR series, at resonance

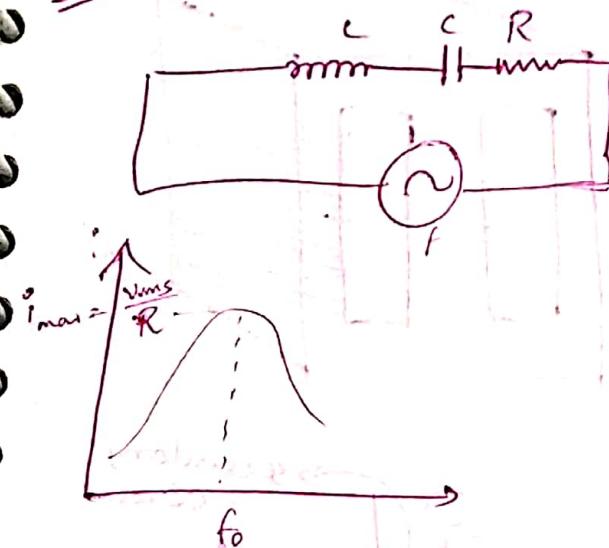

$\rightarrow L$ and C are fixed.

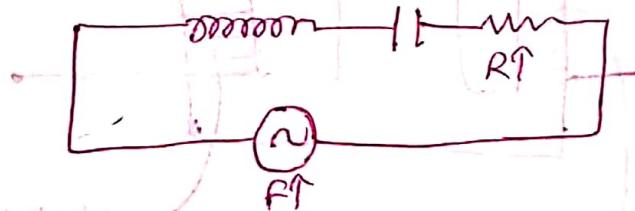

→ Resonance = null load

$$(\text{current with } R=0) \propto V \text{ (at } f_0)$$


$$Z = \sqrt{\left(\omega L - \frac{1}{\omega C}\right)^2 + R^2}$$

$$Z = \sqrt{\left(2\pi f L - \frac{1}{2\pi f C}\right)^2 + R^2}$$

$$\text{at } f = f_0 = \frac{1}{2\pi\sqrt{LC}} \quad X_L = X_C$$

at $f < f_0$, $X_L < X_C$ (Capacitive)

at $f > f_0$, $X_L > X_C$ (Inductive)

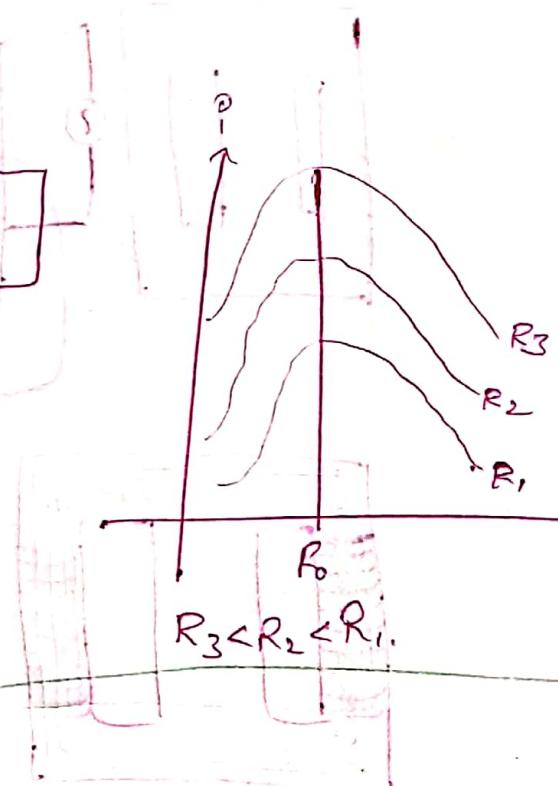

Transf

and Q resonance \propto null load

$$Q_{RL} = \frac{V}{I}$$

= current divided by voltage

$$= \frac{V}{I_R} = \frac{V}{\frac{V}{Z}} = \frac{Z}{V}$$

Q = $\frac{V}{I}$ \Rightarrow $\frac{V}{I}$


$$Q = \frac{V}{I}$$

Q = $\frac{V}{I}$ \Rightarrow $\frac{V}{I}$




$$Q = \frac{V}{I}$$

$$Q_{RL} = \frac{V}{I_R} \quad Q = \frac{V}{I}$$

Transformer

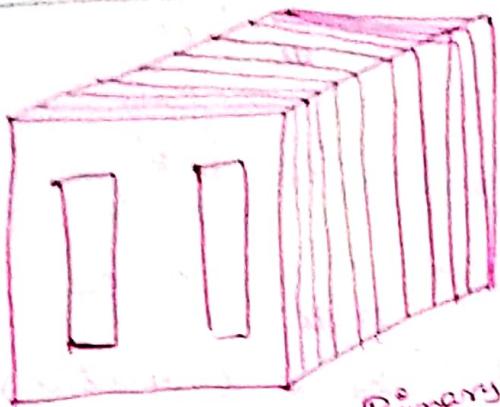

Primary circuit

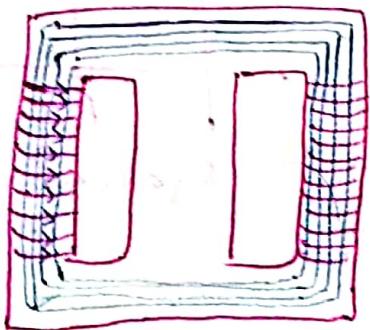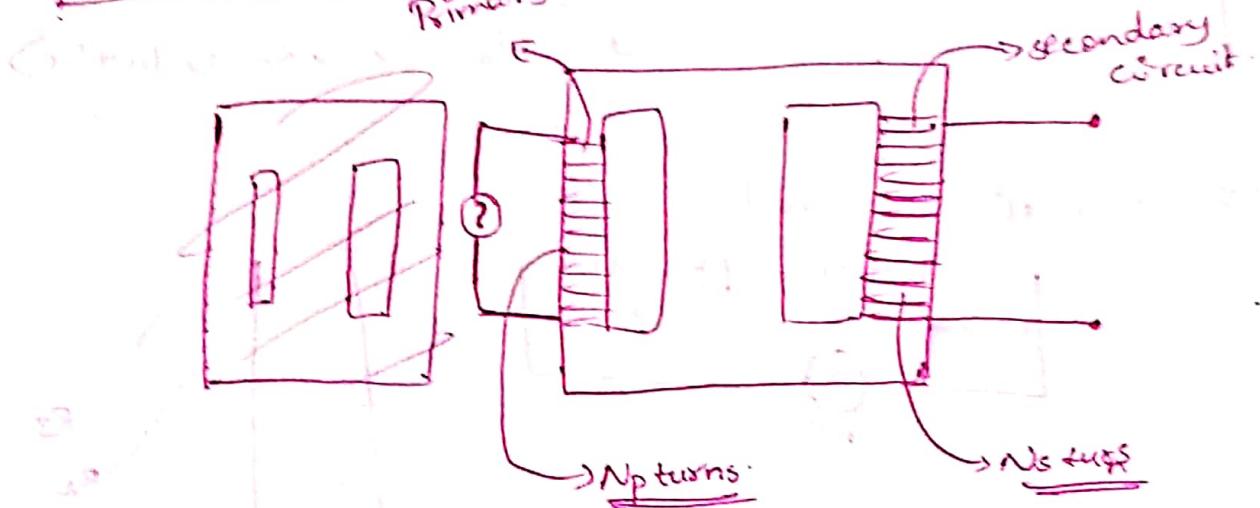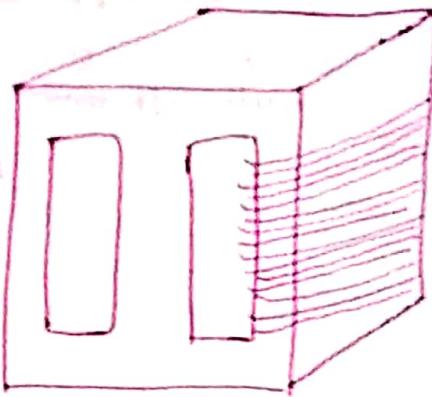

If $N_s = N_p$
 $\Rightarrow E_s = E_p$

If $N_s > N_p$
 $E_s > E_p$ Step up transformer.

If $N_s < N_p$
 $E_s < E_p$ Step down transformer.

$$E_p = \frac{N_p}{N_s} E_s$$

Total flux in primary circuit

$$\Phi_p = N_p \phi \quad (\phi: \text{flux through each loop})$$

emf in the primary circuit

$$E_p = -\frac{d\Phi_p}{dt} = -N_p \frac{d\phi}{dt}$$

Total flux in secondary circuit

$$\Phi = N_s \phi$$

emf in the secondary circuit E_s

$$E_s = -\frac{d\Phi_s}{dt} = N_s \frac{d(\phi)}{dt}$$

Efficiency of transformer = η = $\frac{\text{output power}}{\text{input power}}$

$$\eta = \frac{P_S}{P_P} = \frac{E_S I_S}{E_P I_P} =$$

$$\boxed{\eta = \left(\frac{E_S}{E_P}\right) \left(\frac{I_S}{I_P}\right)}$$

For ideal transformer $\eta = 1$

$$\eta = 1$$

$$\frac{E_S}{E_P} \frac{I_S}{I_P} = 1$$

$$\boxed{\frac{E_S}{E_P} = \frac{I_P}{I_S} = \frac{N_S}{N_P}}$$

Quality Factor

$$\text{Quality Factor} = \frac{X_L}{R} = \frac{X_C}{R} = \frac{1}{\cancel{R}} \frac{1}{\cancel{R}} \sqrt{\frac{L}{C}}$$