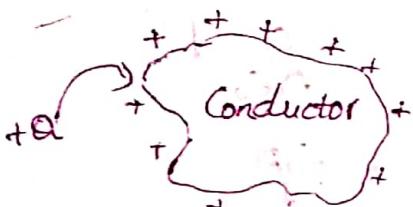


Capacitors

device which stores the energy in form of electric field.

Capacitance :- ability to store the charge by the conductor (or) non-conductor objects

Capacitance of a conductor (isolated conductor) :-



Capacitance of conductor is defined as the ratio of charge to potential


charge \propto potential

$$\alpha \propto V$$

$$\alpha = CV$$

$$C = \frac{Q}{V}$$

↳ capacitance

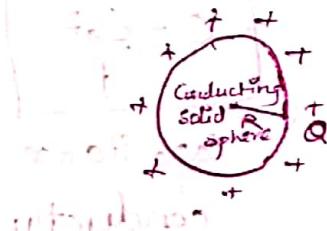

Example

$$V = \frac{Q}{4\pi\epsilon_0 R}$$

$$V = \frac{Q}{4\pi\epsilon_0 R}$$


$$4\pi\epsilon_0 R = \frac{Q}{V}$$

$$C = 4\pi\epsilon_0 R$$

$\propto R$


Capacitance depends only on physical dimension

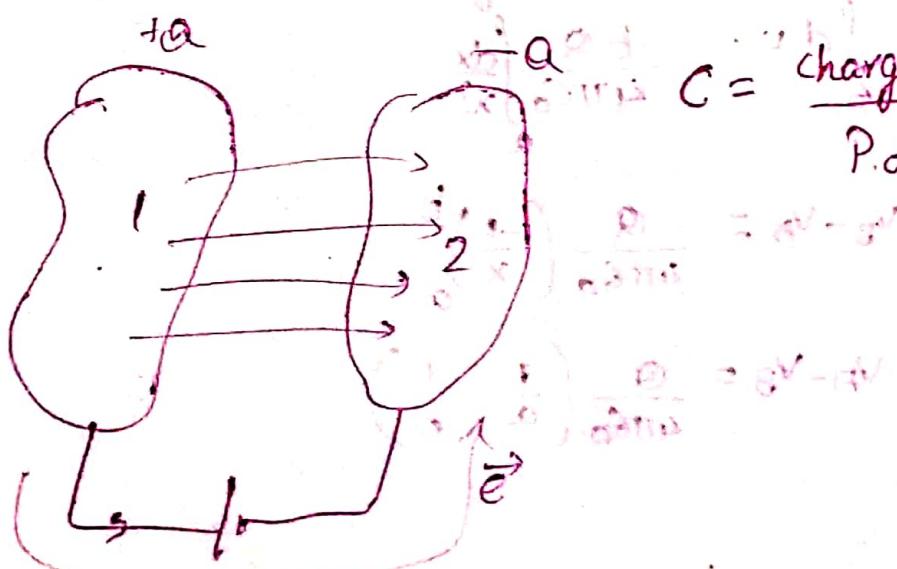Capacitance for combination of conductors :-



$C = \frac{\text{charge on any one conductor}}{\text{P.difference b/w conductors}}$

2) 1st Plate conductor

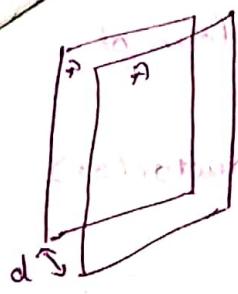

$$(\vec{E})_{\text{net}} = \frac{\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} = \frac{\sigma}{\epsilon_0} = \frac{Q}{A\epsilon_0}$$

$$dV = -\vec{E} \cdot d\vec{r}$$

$$dV = -Ed \cos 90^\circ$$

$$V_B - V_A = -\left(\frac{\sigma}{\epsilon_0}\right) d$$


$$V_A - V_B = \frac{\sigma}{\epsilon_0} d$$

$$\frac{a}{V_A - V_B} = \frac{\epsilon_0 A}{d}$$

$$C = \frac{\epsilon_0 A}{d}$$

capacitance of parallel plate conductor.

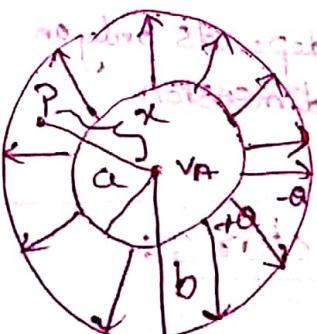Capacitance of spherical capacitor (hollow sphere)



Electric field intensity at point P is

$$E = \frac{Q}{4\pi\epsilon_0 x^2}$$

$$dV = -E (dx) \cos 90^\circ$$

$$\int dV = \frac{-E Q}{4\pi\epsilon_0} \int \frac{dx}{x^2}$$

$$V_B - V_A = \frac{-Q}{4\pi\epsilon_0} \left(\frac{1}{a} - \frac{1}{b}\right)$$


$$V_A - V_B = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{a} - \frac{1}{b}\right)$$

$$V_B - V_A = \frac{Q}{2\pi\epsilon_0} \left(\frac{b-a}{b+a} \right)$$

$$\frac{Q}{V_B - V_A} = 4\pi\epsilon_0 \left(\frac{b-a}{b+a} \right)$$

$$C = 4\pi\epsilon_0 \left(\frac{b-a}{b+a} \right)$$


2nd Method

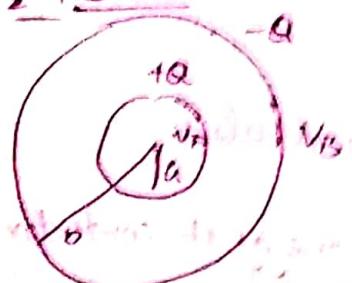

$$V_B - V_A = \left(\frac{Ka}{a} - \frac{Ka}{b} \right) = \left(\frac{K}{b} - \frac{K}{a} \right)$$

$$V_B - V_A = KQ \left(\frac{b-a}{ba} \right)$$

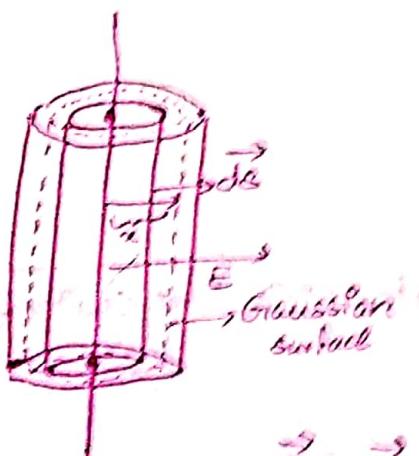We know the potential $V = \frac{Q}{C} = \frac{Q}{4\pi\epsilon_0 (ba)} + C$



$$\oint \vec{E} \cdot d\vec{s} = \frac{Q}{\epsilon_0}$$

$$E \cdot 2\pi al = \frac{Q}{\epsilon_0}$$

$$E = \frac{Q}{2\pi al\epsilon_0}$$

$$\oint \vec{E} \cdot d\vec{s} = \int_{V_B}^{V_A} \int_a^b \frac{Q}{2\pi al\epsilon_0} da dl$$


$$\text{Hence, } V_B - V_A = \frac{Q}{2\pi al\epsilon_0} \ln \left(\frac{b}{a} \right)$$

$$V_B - V_A = \frac{Q}{2\pi al\epsilon_0} \ln \left(\frac{b}{a} \right)$$

$$C = \frac{2\pi al\epsilon_0}{\ln \left(\frac{b}{a} \right)}$$

Important points regarding parallel plate conductor


- ① initially uncharged

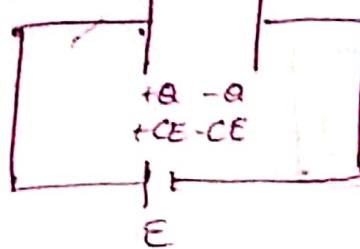

$$C = \frac{Q}{E}$$

$$Q = EC$$

- ②

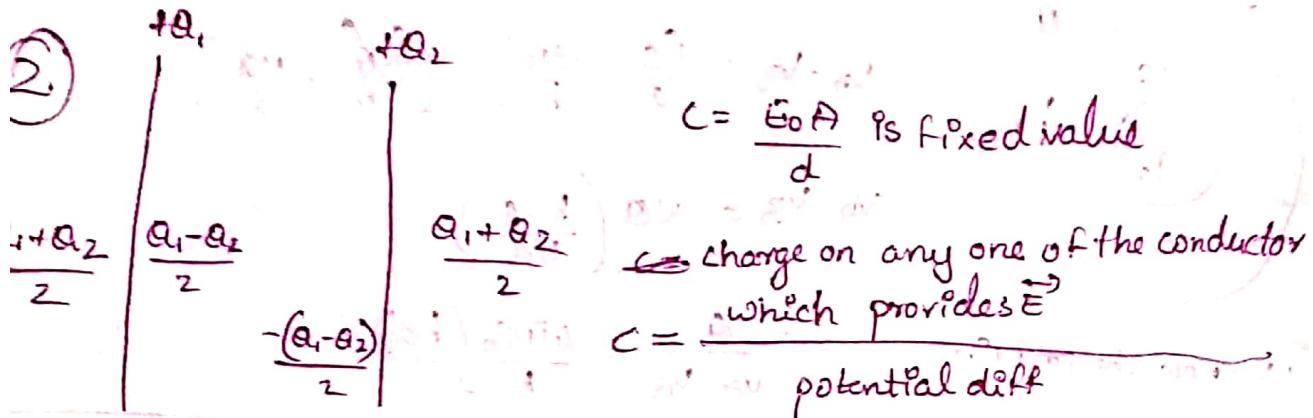

$$C = \frac{\epsilon_0 A}{d}$$


charge on any one of the conductor which provides E

$$C = \frac{Q_1 - Q_2}{2 \Delta V}$$

$$C = \frac{Q_1 - Q_2}{2 \Delta V}$$

$$\Delta V = \frac{Q_1 - Q_2}{2C}$$

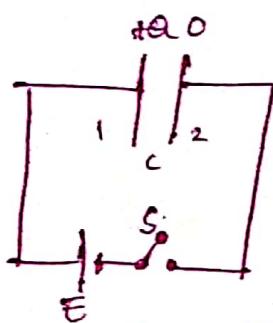- 1) Find the charge on the first plate after the switch is closed.




$$C = \frac{Q}{V} = \frac{\epsilon_0 A}{d}$$


$$Q = VC$$

$$V = \frac{KQ}{R}$$

Before closing switch

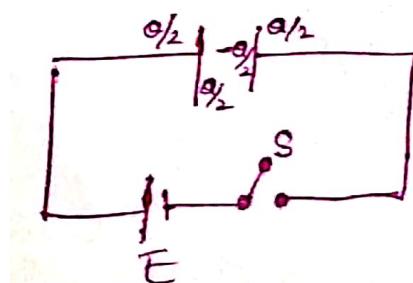

After closing switch

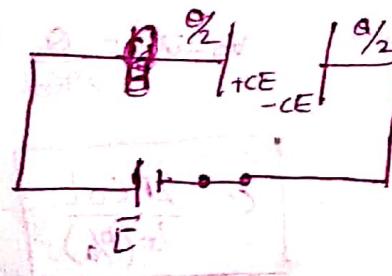

If $q < C\epsilon_0$ charge supplied by battery is $C\epsilon_0 \cdot \frac{q}{\epsilon_0}$


If $q > C\epsilon_0$ charge supplied by battery is $\epsilon_0 \cdot C\epsilon_0$

If $\frac{q}{2} < C\epsilon_0$ charge supplied by battery is $\epsilon_0 \cdot C\epsilon_0$

After closing switch Pad across capacitor remains.

∴ Final charge on 1st plate = $\frac{q}{2} + \epsilon_0 C\epsilon_0$

Force acting b/w two plates of capacitor

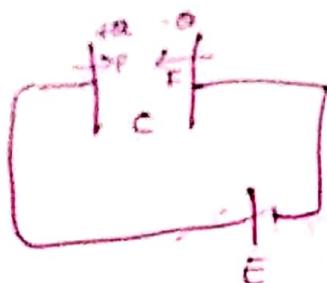

$$|F| = \frac{Q}{2\epsilon_0 C_0}$$

Force acting on 2nd plate is $|F| = QE$

$$|F| = Q \left(\frac{1}{2\epsilon_0 C_0} \right)$$

$$|F| = \frac{Q^2}{2\epsilon_0 C_0}$$

is independent of distance b/w plates

Force acting

Energy stored in capacitor

Work required to add dq charge is $dw = (da) \left(\frac{q}{C} \right)$

Total work required to get the charge of Q

$$\text{is } W_{\text{ext}} = \int dw = \int dq \left(\frac{q}{C} \right)$$


$$W_{\text{ext}} = \frac{1}{C} \left(\frac{q^2}{2} \right)_0$$

$$W_{\text{ext}} = \frac{Q^2}{2C}$$

Energy stored in the capacitor is $\frac{1}{2}CE^2$

$$U = \frac{Q^2}{2C}$$
$$= \frac{CE^2}{2C}$$
$$= \frac{1}{2}CE^2$$

Note:-

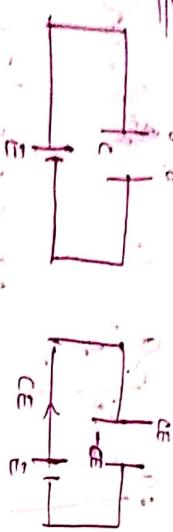

Energy stored in the capacitor $P_S = U = \frac{1}{2}CE^2$

Charge supplied by battery is $Q = CE$

Work done by battery is $W_b = (\text{Charge})(\text{P.d})$

$$W_b = CE \cdot E$$

Work done by battery is $W_b = CE^2$.
Heat generated in system = $W_{\text{battery}} - Q$ (increase in energy)

$$\text{Heat generated} = CE^2 - \frac{1}{2}CE^2$$
$$= \frac{1}{2}CE^2$$

It is observed that the energy stored in the capacitor is equal to the energy supplied by the battery.

Series
Connection



$$Q = \frac{V}{R} t$$

$$P_{\text{battery}}$$


$$P_{\text{battery}}$$

Connection of Capacitors

Series connection

→ isolated plates

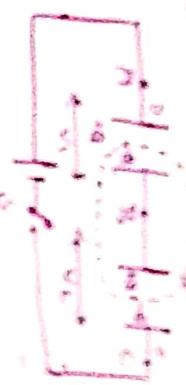
Charge on isolated plates
always remains same



$$V_1 = V_B - V_A$$

$$V_2 = V_B - V_C$$
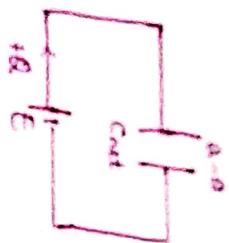
$$V_1 + V_2 = V_B - V_A - V_B + V_C = V_C - V_A$$



$$V_1 + V_2 = E$$


$$Q = C_{\text{tot}} E$$

$$Q = C_1 V_1$$

$$Q = C_2 V_2$$

$$\frac{1}{C_{\text{tot}}} = \frac{1}{C_1} + \frac{1}{C_2} \quad [\text{For series}]$$

Parallel connection

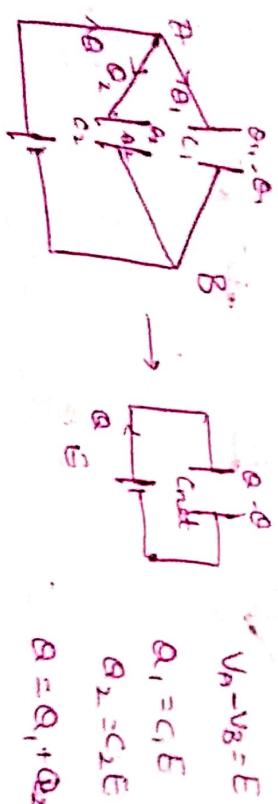

$$V_B = E$$

$$V_1 + V_2 = E$$

$$Q = C_{\text{tot}} E$$


$$Q_1 = C_1 E$$

$$Q_2 = C_2 E$$

$$Q = Q_1 + Q_2$$


$$C_{\text{tot}} = C_1 + C_2 \quad [\text{For parallel}]$$
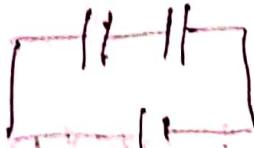
$$\sqrt{\left(\frac{C_1 C_2}{C_1 + C_2}\right)} = \frac{Q}{V}$$



$$Q = \frac{C_1 V_1}{C_1 + C_2}$$
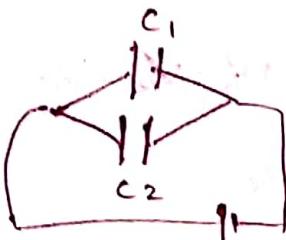
$$V_1 = \sqrt{\left(\frac{C_2}{C_1 + C_2}\right)} V, V_2 = \sqrt{\left(\frac{C_1}{C_1 + C_2}\right)} V$$



$$\frac{C_1 + C_2}{V} = \frac{Q}{V}$$


$$Q_1 = C_1 V$$

$$Q_1 = \left(\frac{C_1 + C_2}{V}\right) C_1 = \frac{Q C_1}{C_1 + C_2}$$

$$Q_2 = \left(\frac{C_1 + C_2}{V}\right) C_2 = \frac{Q C_2}{C_1 + C_2}$$

Finding net capacitance of circuit

a)

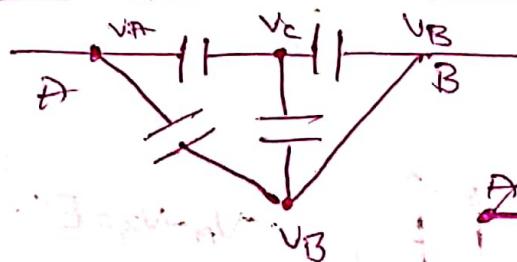


$$\therefore \frac{5C}{3}$$


$$\frac{2C}{3} + C$$

b)

$$2C + 3C = 5C$$

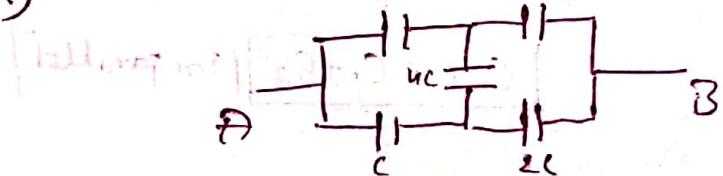

$$C_{net} = 2C$$

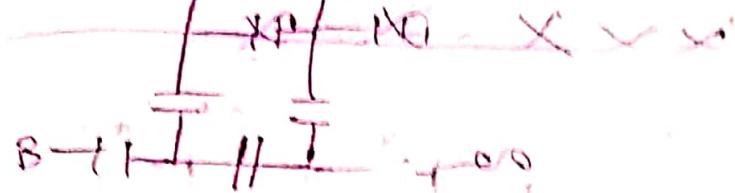


$$\frac{1}{x} = \frac{1}{2C} + \frac{2}{C}$$

$$6 \cdot C^2 + 12Cx$$

$$6 \cdot \left(\frac{C}{2x}\right)^2 + \frac{1}{x} + \frac{2}{C}$$


$$6 \left(\frac{C}{2x}\right)^2 = \frac{2}{C}$$

$$2x^2 + \frac{2}{C} - 1 = 0$$

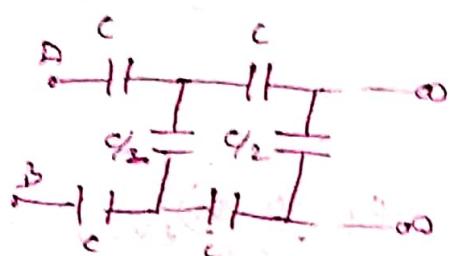

$$\frac{-2C + \sqrt{4C^2 + 12C^2}}{4}$$

$$\frac{-2C + 4C}{4} = \frac{C}{2}$$

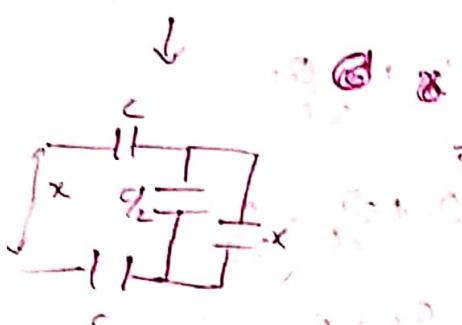


$$\frac{1}{x} = \frac{1}{C} + \frac{1}{C} + \frac{1}{\frac{C}{2} + x}$$

$$\frac{1}{2Cx} = \frac{2C + 2x}{C(C + 2x)}$$


$$4x^2 + 2Cx - C^2 = 0$$

$$x = \left(\frac{\sqrt{5}-1}{2}\right)C$$


a) Potential drop across capacitor

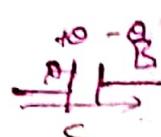
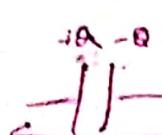
$$\text{Potential drop } V_B - V_A = -(V_A - V_B) = \frac{Q}{C}$$



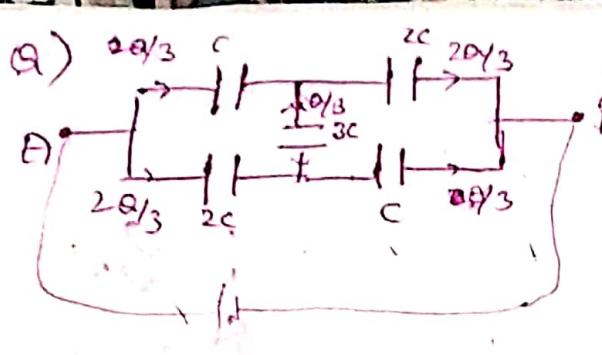
$$\text{Potential drop } V_A - V_B = \frac{Q}{C}$$



As these are isolated total charge is 0.

$$C_{\text{net}} = \frac{Q}{V}$$

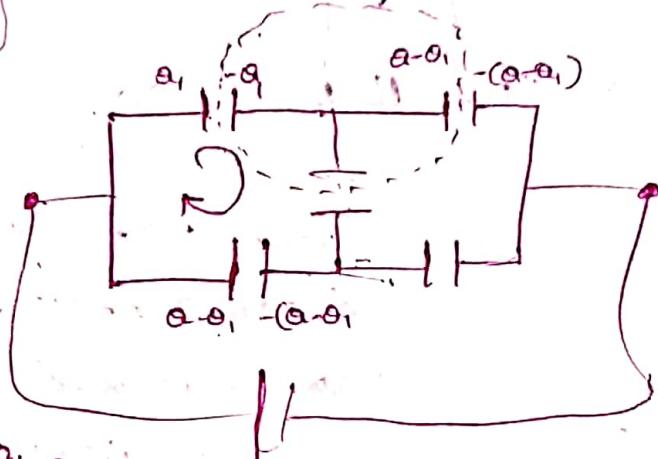

$$-\frac{Q_1}{C} + \frac{Q-2Q_1}{2C} + \frac{Q-Q_1}{2C} = 0$$

$$\left(\frac{Q}{3C} + \frac{Q}{2C}\right) - \left(\frac{Q_1}{C} + \frac{2Q_1}{3C} + \frac{Q_1}{2C}\right) = 0$$

$$\frac{5Q}{6C} - \frac{13Q_1}{6C} = 0$$

$$5Q = 13Q_1$$

$$-\frac{Q_1}{C} - \frac{(Q-Q_1)}{2C} + V = 0$$

$$V = \frac{Q_1}{C} + \frac{Q-Q_1}{2C}$$

$$V = \frac{Q_1}{C} + \frac{Q}{2C} - \frac{Q_1}{2C}$$

$$V = \frac{Q_1}{2C} + \frac{Q}{2C}$$

$$V = \frac{5Q}{13} + \frac{Q}{2C}$$


$$V = \frac{9Q}{13C}$$

$$\frac{Q}{V} = \frac{13C}{9}$$

$$C_{\text{net}} = \frac{13C}{9}$$

(a)

Q)

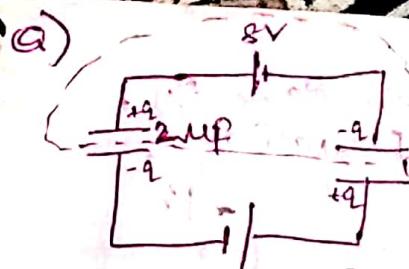


Find the charge on 1μF capacitor

$$-8 + \frac{q}{2\mu F} - 4 + \frac{q}{2\mu F} = 0$$

$$\frac{3q}{2\mu F} = 12 \text{ Volts}$$

$$q = 8 \mu C$$

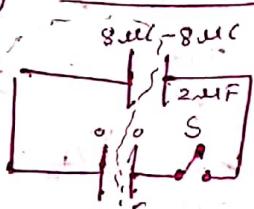Q) Charge distribution between capacitors.




$$\frac{8-x}{2} = \frac{x}{4}$$

$$\frac{(8-x)}{2} = \frac{x}{4\mu F}$$

$$16 - 2x = x$$

$$x = \frac{16}{3}$$

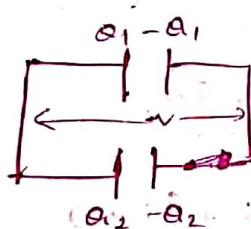

$$\theta_1 + \theta_2 = 8$$

$$\frac{\theta_1}{2} = \frac{\theta_2}{4}$$

$$2\theta_1 = \theta_2$$

$$\theta_1 + 2\theta_1 = 8$$

$$\theta_1 = \frac{8}{3} \mu C$$

$$\theta_2 = \frac{16}{3} \mu C$$


$$\text{Loss of energy} = 0i - U_f$$

$$= \frac{1}{2} (2)(2)^2 - \left(\frac{1}{2} \times 2 \times \left(\frac{16}{3}\right)^2 + \frac{1}{2} \times 4 \times \left(\frac{4}{3}\right)^2 \right)$$

$$= \frac{1}{2} \times 2 \times 16 - \frac{1}{2} \times 6 \times \frac{16}{9}$$

$$= \frac{9 \times 16}{9} - \frac{16 \times 16}{9}$$
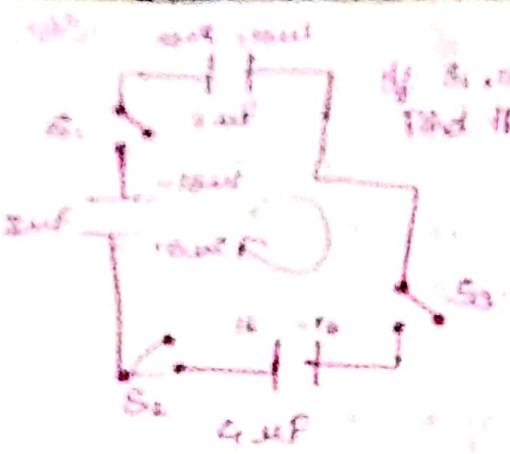
$$\text{Loss in energy} = \frac{16 \times 62}{9} = \frac{32}{3} \mu J$$



If S₁, S₂, S₃ are closed simultaneously,
Find the charge on Bus capacitor.

$$\begin{aligned} Q_1 + Q_2 &= -5 \rightarrow ① \\ -Q_2 + Q_3 &= 31 \rightarrow ② \\ -Q_3 - Q_1 &= -26 \rightarrow ③ \end{aligned}$$

$$\begin{aligned} Q_1 + Q_2 &= -5 \\ Q_2 - Q_3 &= -31 \\ Q_1 + Q_3 &= 26 \end{aligned}$$

$$Q_1 + Q_2 = -5$$

$$Q_1 - Q_3 = -31$$

$$Q_1 + Q_3 = 26$$

$$Q_2 - Q_1 = -26$$

$$\begin{aligned} Q_1 + Q_2 &= -5 \\ -Q_2 + Q_3 &= 31 \\ Q_3 + Q_1 &= 26 \\ \hline Q_3 &= 31 - 21 = 10 \end{aligned}$$

$$\begin{aligned} Q_2 - Q_1 &= 26 \\ Q_1 + Q_2 &= -5 \\ 2Q_2 &= 21 \rightarrow Q_2 = \frac{21}{2} \\ Q_2 &= 10.5 \end{aligned}$$

$$\begin{aligned} \frac{Q_1}{2} - \frac{Q_2}{6} - \frac{Q_3}{3} &= 0 \\ \frac{Q_1}{2} + \frac{Q_2}{4} + \frac{Q_3}{3} &= 0 \end{aligned}$$


④

$$6Q_1 + 3Q_2 + 4Q_3 = 0$$

$$(Q_3 - 5)6 + (Q_3 - 3)3 + 4(Q_3) = 0$$

$$Q_3 = \frac{123}{13} \mu C$$


a)

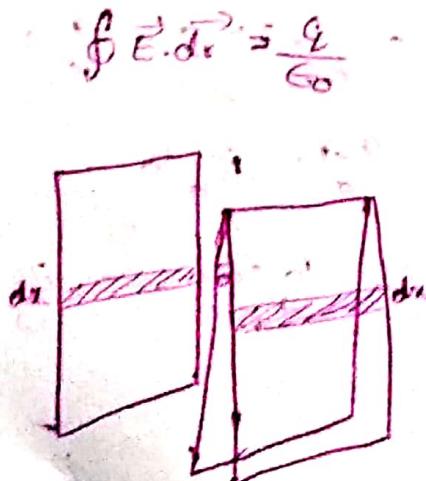

$$f E \cdot d = \frac{q}{\epsilon_0}$$

$$dx \rightarrow \frac{dc}{d+x\tan\theta}$$
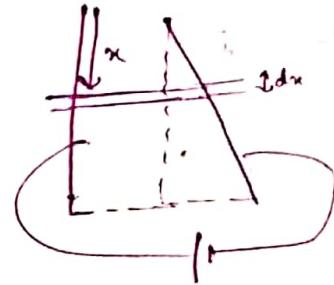
$$dc = \frac{\epsilon_0 (1dx)}{d+x\tan\theta}$$



Net capacitance of capacitors is


$$C_{\text{net}} = dc_1 + dc_2 + dc_3 + \dots + dc_n$$

$$= \frac{\epsilon_0 (1dx)}{d+x\tan\theta} \cdot L$$

$$= \epsilon_0 L \frac{1}{\tan\theta} \left(\ln \left(\frac{d+xt\tan\theta}{d} \right) \right)$$

$$C_{\text{net}} = \frac{\epsilon_0 L}{\tan\theta} \left(\ln \left(\frac{d+L\tan\theta}{d} \right) \right)$$

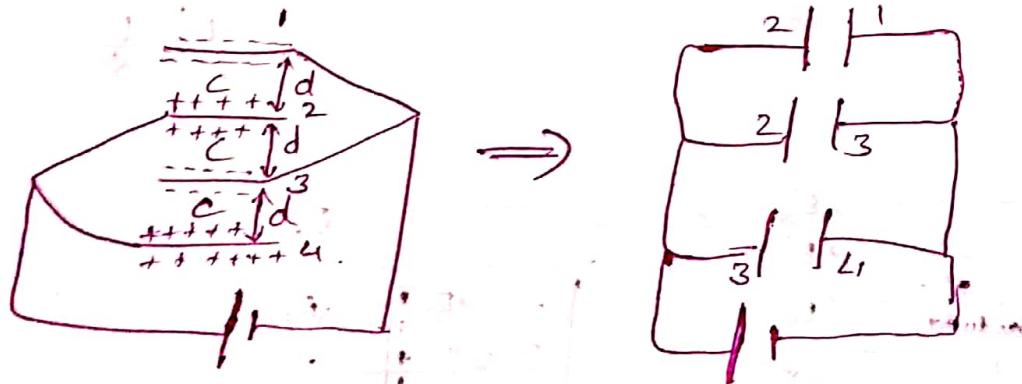Finding Capacitance when plates combination is given :-



$$C_{\text{net}} = 3C$$

$$C_{\text{net}} = \frac{3A\epsilon_0}{d}$$



$$A = \pi r^2$$

$$d = \frac{h}{4}$$

$$C = \frac{\epsilon_0 \pi r^2 h}{d}$$

$$C = \frac{\epsilon_0 \pi r^2 h}{\frac{h}{4}}$$

$$C = 4\epsilon_0 \pi r^2$$

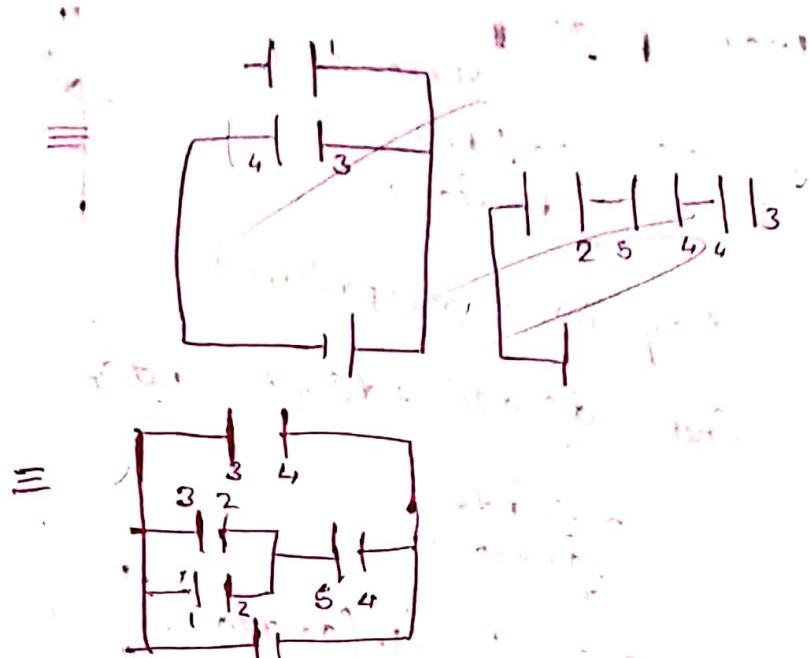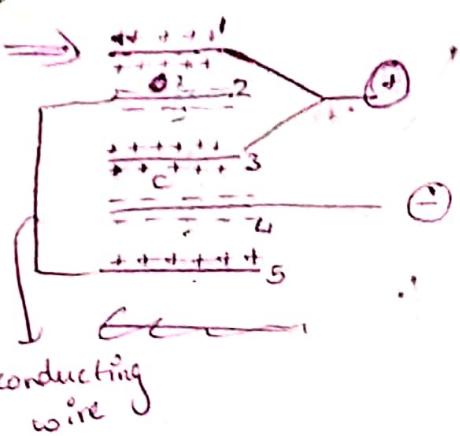


$$C_{\text{net}} = \frac{5C}{3} = \frac{5\epsilon_0 A}{3d}$$

Capacitance with dielectric material

$$\Rightarrow +Q - \frac{\text{vacuum}}{r} E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$E' = \frac{Q}{4\pi K\epsilon_0 r^2}$$

$$E' = \frac{E}{K}$$

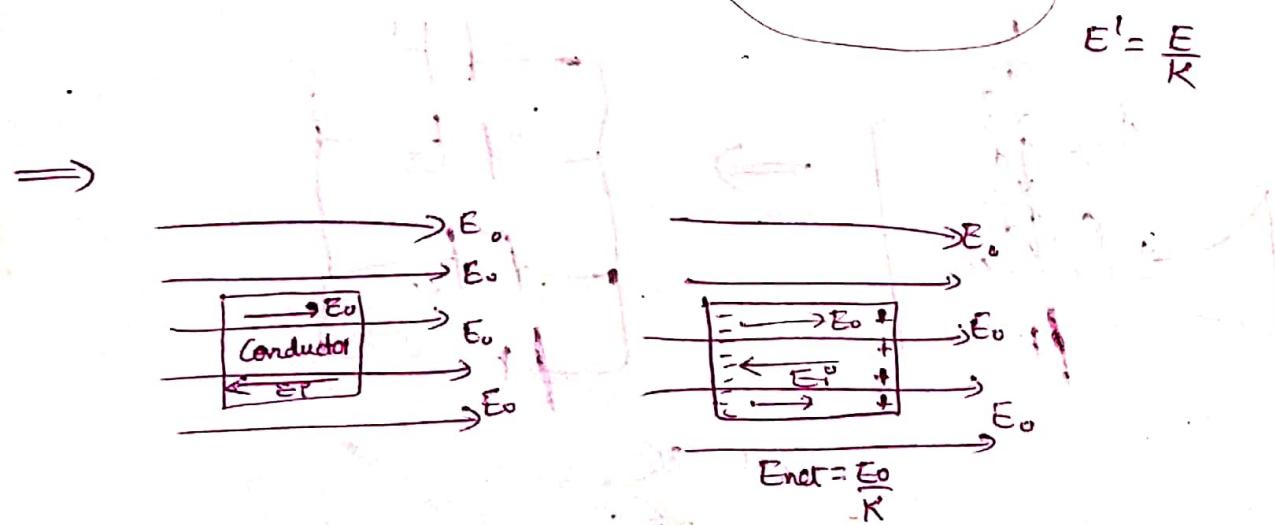



$$E_{\text{net}} = E_0 - E_i$$

$$\frac{E_0}{K} = E_0 - E_i$$

$$E_i^0 = E_0 - \frac{E_0}{K}$$

$$E_i^i = E_0 \left(1 - \frac{1}{K}\right)$$

Capacitance of 2 Plates

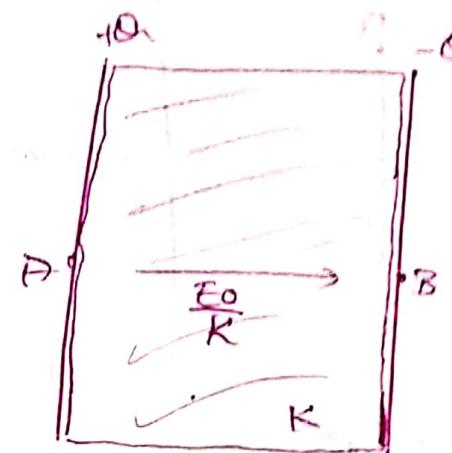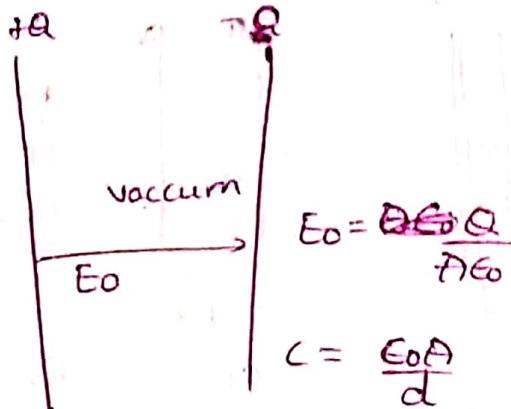


$$V_A - V_B = \frac{Q}{\epsilon_0 K d}$$

$$\Delta V = \frac{Qd}{K\epsilon_0 A}$$

$$\frac{Q}{\Delta V} = \frac{K\epsilon_0 A}{d}$$

$$C_{\text{with dielectric}} = K C_{\text{without dielectric}}$$

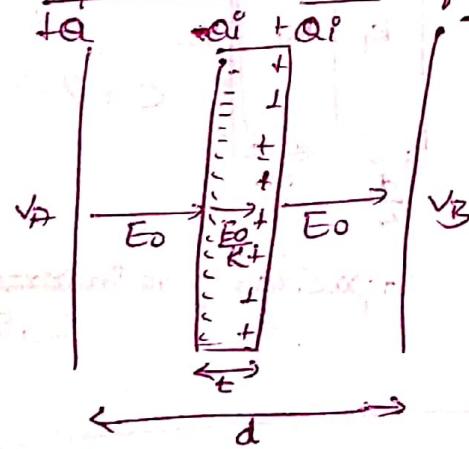Capacitance with partially filled dielectric



$$V_A - V_B = E_0 (d-t) + \frac{E_0 t}{K}$$

$$\Delta V = E_0 \left(d-t+\frac{t}{K} \right)$$

$$\frac{Q}{\Delta V} = \frac{A}{\epsilon_0} \left(d-t+\frac{t}{K} \right)$$

$$\frac{Q}{\Delta V} = \frac{\epsilon_0 A}{d-t+t/K}$$

Induced electric field

$$E_i = E_0 \left(1 - \frac{1}{K} \right)$$


$$\frac{Q_i}{\epsilon_0} = \frac{Q}{\epsilon_0} \left(1 - \frac{1}{K} \right) \Rightarrow Q_i = Q \left(1 - \frac{1}{K} \right)$$

$$C = \frac{\epsilon_0 A}{d-t+t/K}$$

is independent of position of dielectric

Induced charge on surface of non conducting material.

All concate method

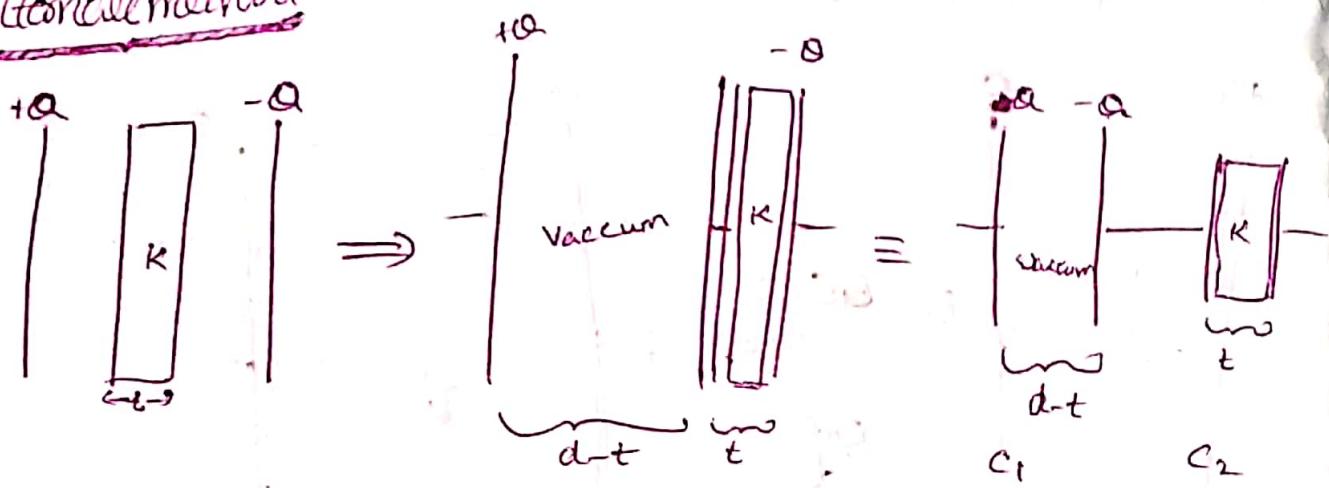

$$C_1 = \frac{\epsilon_0 A}{d-t}$$

$$C_2 = \frac{K \epsilon_0 A}{t}$$

$$C_{\text{net}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$= \frac{\frac{\epsilon_0 A}{d-t} \frac{K \epsilon_0 A}{t}}{\frac{\epsilon_0 A}{d-t} + \frac{K \epsilon_0 A}{t}}$$

$$C_{\text{net}} = \frac{\epsilon_0 A}{d-t + t/K}$$


C_1 & C_2 are in series

$$C_1 = \frac{4 K_1 \epsilon_0 A}{d} \quad C_2 = \frac{4 K_2 \epsilon_0 A}{3d}$$

$$C_{\text{net}} = \frac{\frac{4 K_1 \epsilon_0 A}{d} \times \frac{4 K_2 \epsilon_0 A}{3d}}{3d}$$

$$= \frac{16 K_1 K_2 \epsilon_0^2 A^2}{9d^3}$$
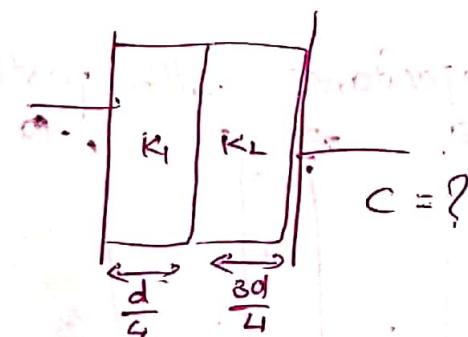
$$C_{\text{net}} = \frac{(4 K_1 K_2) \epsilon_0 A}{3(K_1 + K_2) d}$$




Capacitors are in ~~parallel~~ series

$$C_1 = \frac{8 K_1 \epsilon_0 A}{d/2}$$

$$C_2 = \frac{8 K_2 \epsilon_0 A}{3d/2}$$

total thickness
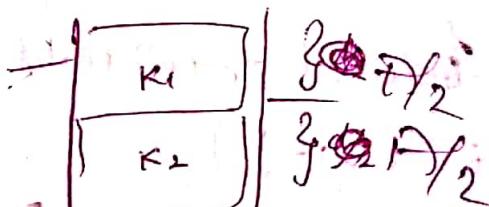
$$C_{\text{net}} = C_1 + C_2 = \frac{8 \epsilon_0 A}{d/2} (K_1 + K_2)$$



Capacitors are in ~~parallel~~ series

$$C_1 = \frac{2K_1 A \epsilon_0}{d}$$

$$C_2 = \frac{K_2 A \epsilon_0}{\frac{d}{2}} = \frac{K_2 A \epsilon_0}{\frac{d}{2}}$$

$$C_3 = \frac{K_3 A \epsilon_0}{\frac{d}{2}}$$

C_2, C_3 in parallel

$$C_{23} = \frac{(K_2 + K_3) A \epsilon_0}{d}$$



C_1, C_{23} is in series

$$\frac{1}{C_{\text{net}}} = \frac{d}{2K_1 A \epsilon_0} + \frac{d}{(K_2 + K_3) A \epsilon_0}$$

~~$$\frac{1}{C_{\text{net}}} = \frac{d}{A \epsilon_0} \left(\frac{K_2 + K_3 + 2K_1}{2K_1(K_2 + K_3)} \right)$$~~

~~$$C_{\text{net}} = \frac{A \epsilon_0}{d} \left(\frac{2K_1(K_2 + K_3)}{2K_1 + K_2 + K_3} \right)$$~~

(a)

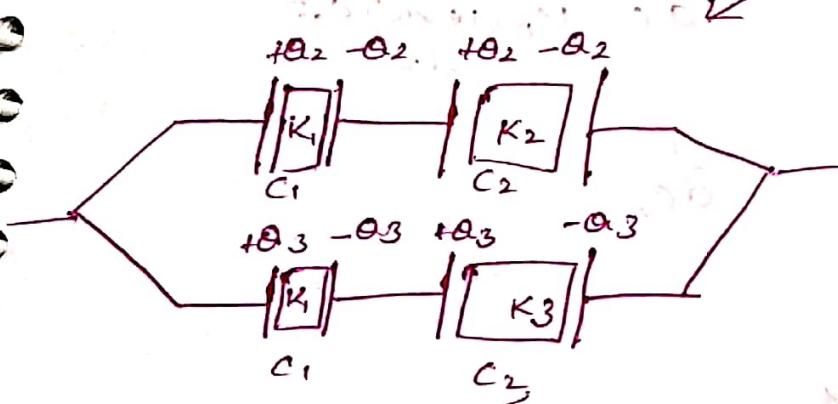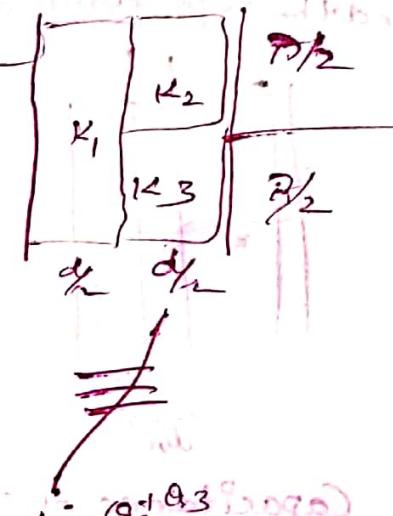


charge density must remain constant. So it is divided into 2 capacitors

$$C_{\text{up}} = \left(\frac{K_1 K_2}{K_1 + K_2} \right) \frac{A \epsilon_0}{d} \quad C_{\text{do}} = \left(\frac{K_1 K_3}{K_1 + K_3} \right) \frac{A \epsilon_0}{d}$$


$$C_{\text{net}} = C_{\text{up}} + C_{\text{down}}$$
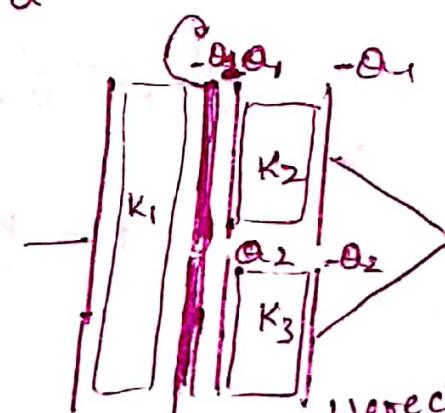
$$C_{\text{net}} = \left(\frac{K_1 K_2}{K_1 + K_2} + \frac{K_1 K_3}{K_1 + K_3} \right) \frac{A \epsilon_0}{d}$$



Here charge density is not same so it should be broken into two

Q)

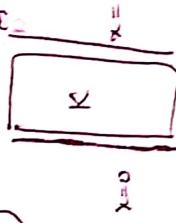


$$\frac{dV}{dx} = \frac{E_0}{K_0(1+\alpha x)} \frac{dE}{dx}$$

If dielectric constant is variable which is $K = K_0(1+\alpha x)$ where

K_0 and α are constants.

Find the capacitance of capacitors

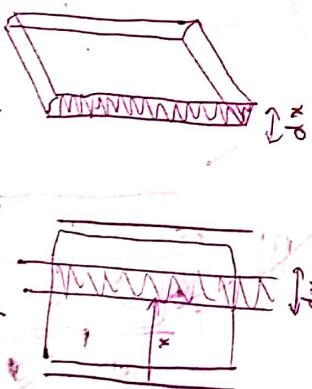

$$dV = \frac{E_0}{K_0} \left[\ln(1+\alpha x) \right] dx$$

$$dV = \frac{E_0}{K_0} \left[\ln(1+\alpha d) \right] dx$$

$$V = \frac{Q}{A \epsilon_0 K_0} \left[\ln(1+\alpha d) \right]$$

$$C = \frac{Q}{V} = \frac{K_0 \epsilon_0 A \alpha}{\ln(1+\alpha d)}$$

Capacitance of small part $dc = \frac{K_0 \epsilon_0 (dx)}{d^m}$

$$dc = K_0 (1+\alpha x) \epsilon_0 dx$$


Net capacitance,

$$\frac{1}{C_{net}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_m}$$

$$\frac{1}{C_{net}} = \frac{1}{\int_0^d \frac{dx}{K_0(1+\alpha x)} \epsilon_0 A}$$

$$\frac{1}{C_{net}} = \frac{1}{K_0 \epsilon_0 A \alpha} \left(\ln(1+\alpha d) \right) d$$
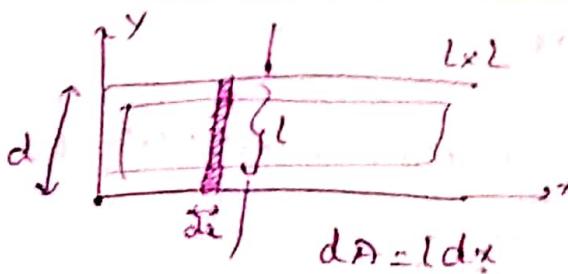
$$C_{net} = \frac{K_0 \epsilon_0 A \alpha}{\ln(1+\alpha d)}$$



if dielectric constant of

material changes as $K_a = K_0 x$.
Find the capacitance of
a capacitor

$$dC = \frac{K_o E_o}{dd} \times l \, da$$

$$C_{\text{net}} = C_1 + C_2 + C_3 + \dots + C_{\text{net}}$$


$$C_{net} = \int \frac{K_0 f_0 l}{\sigma t} \ x \, dx$$

$$= \frac{k_0 \epsilon_0 l}{d} \left[\frac{x^2}{2} \right]_0^l$$

$$= k_0 \epsilon_0 l \cdot l^2$$

$$C_{nit} = \frac{K_0 G_0 L^3}{2d}$$

Notes

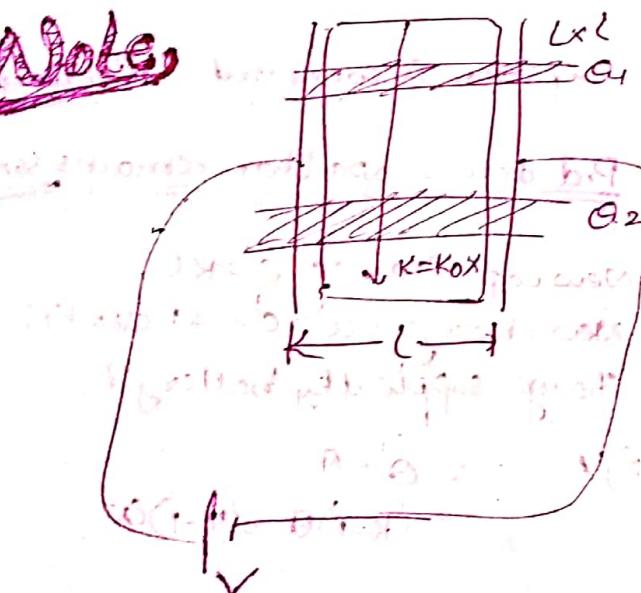

Kaswe go down

dc, \angle dc2

P.d. across dc_1 and dc_2 are same

$$Q_1 < Q_2$$

$\sigma_1 < \sigma_2$ first and second

Effect of dielectric in capacitors

Case I if battery is disconnected and dielectric is kept inside capacitor.



\rightarrow \rightarrow

Isolated capacitor

\rightarrow \rightarrow

Q remains same in an isolated capacitor

New capacitance $= KC$

$$\text{New } V = V' = \frac{V}{K}$$

Initial energy stored in capacitor $= \frac{1}{2} CV^2$


$$\begin{aligned} \text{Final energy stored in capacitor} &= \frac{1}{2} C' V'^2 \\ &= \frac{1}{2} K C \frac{V^2}{K^2} \\ \text{final energy} &= U_f = \frac{1}{K} U_i \end{aligned}$$

$$\text{Energy lost} = U_i - U_f$$

$$\begin{aligned} &= U_i - \frac{U_i}{K} \\ &= \frac{1}{2} CV^2 \left(1 - \frac{1}{K}\right) \end{aligned}$$

Case II

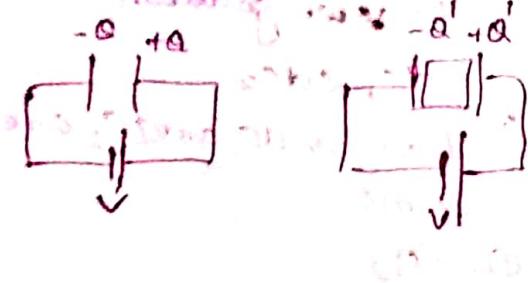Dielectric is inserted when capacitor is connected to battery



P.d across capacitor remains same

$$\text{New capacitance } C' = KC$$

$$\text{New charge} = Q' = C'V = KCV = KQ$$


charge supplied by battery is

$$\begin{aligned} \text{Work done by battery} &= W_b = (Q_{\text{sup}})V \\ W_b &= (K-1)CV \cdot V \\ &= (K-1)CV^2 \end{aligned}$$

Increase in energy of capacitor $\Delta V = U_f - U_i$

$$\begin{aligned} &= \frac{1}{2} (KC)V^2 - \frac{1}{2} CV^2 \\ &= \frac{1}{2} (K-1)CV^2 \end{aligned}$$
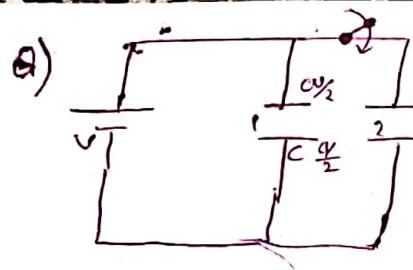
$$\text{Energy lost} = \frac{1}{2} (K-1)CV^2$$



Initially switch is closed position
Now switch is open and dielectric of dielectric constant $K=3$ is kept inside capacitor 2. Find the ratio of initial and final energies.


$$U_i^0 = \frac{1}{2} CV \left(\frac{CV}{2C} \right)^2 + \left(\frac{CV}{2C} \right)^2 = \frac{CV^2}{8} + \frac{CV^2}{8} = \frac{CV^2}{4}$$

$$U_{f1} = \frac{K^2 CV^2}{4 \times 2C} = \frac{K^2 V^2}{8}$$

$$Q' = \frac{KCV}{2} = \frac{K^2 V^2}{8} = \frac{9V^2}{8}$$


$$U_{f2} = \frac{1}{2} \left(\frac{CV}{2} \right)^2 \frac{1}{2KC} = \frac{CV^2}{8K} = \frac{CV^2}{24}$$

initially

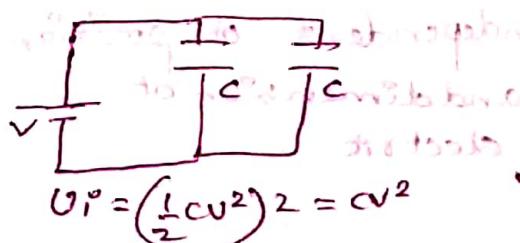

$$U_i^0 = \left(\frac{1}{2} CV^2 \right) 2 = CV^2$$


finally

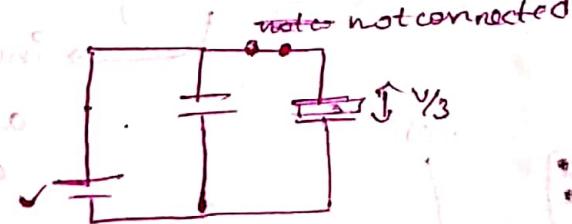

$$U_f = \frac{1}{2} CV^2 + \frac{1}{2} (3C) \left(\frac{V}{3} \right)^2 = \frac{1}{2} CV^2 + \frac{CV^2}{6} = \frac{2CV^2}{3}$$

$$\frac{U_f}{U_i^0} = \frac{2}{3}$$

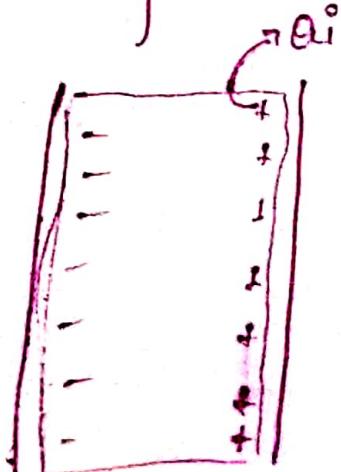(b) Force and stress acting on dielectric in capacitor



$$E_0 = \frac{\sigma}{\epsilon_0} = \frac{Q}{A\epsilon_0}$$

$$Q_i = Q \left(1 - \frac{1}{K} \right)$$

Net force acting on dielectric is zero

Force acting on one surface of dielectric

$$\text{i.e. } F = QE$$

$$F = Q E_0$$

$$F = Q \left(1 - \frac{1}{R}\right) \left(\frac{a}{R E_0}\right)$$

$$F = \frac{a^2}{R E_0} \left(1 - \frac{1}{R}\right)$$

Stress acting on the dielectric σ_s


$$= \frac{F}{\text{Area}}$$

$$= \frac{a^2}{R E_0} \left(1 - \frac{1}{R}\right)$$

$$= \frac{a^2}{R^2 E_0} \left(1 - \frac{1}{R}\right)$$

$$\boxed{\text{stress} = \frac{a^2}{R^2 E_0} \left(1 - \frac{1}{R}\right)}$$


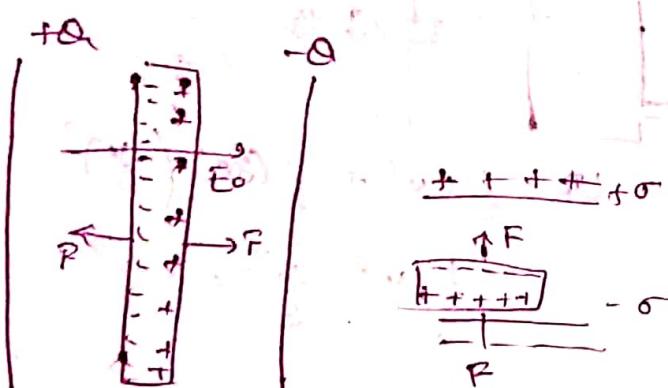
Independent of position and dimension of dielectric





$$E_0 = \sigma / (2 \epsilon_0)$$

$$R$$

end effect/bringing effect

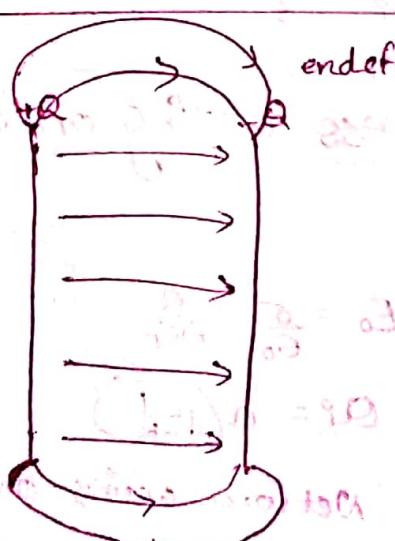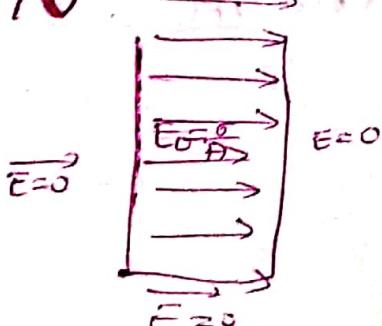

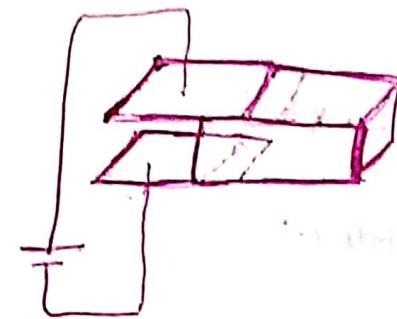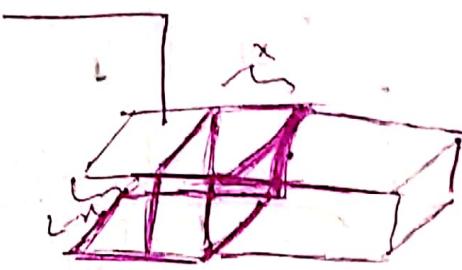Assumption
Assume the dielectric slab to be thin and no finite area




$$F = -\frac{dU}{dx} \quad \text{Capacitance of capacitor}$$

$$C = C_1 + C_2$$

$$C = \frac{\epsilon_0 (L-x) b}{a} + \frac{K \epsilon_0 (bx)}{d}$$

$$C = \frac{\epsilon_0 b}{d} (L-x + Kx)$$
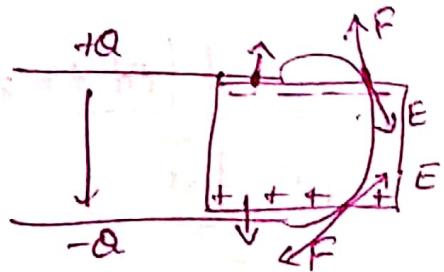
$$\boxed{C = \frac{\epsilon_0 b}{d} (L + (K-1)x)}$$



$$F = \left(\frac{dU}{dx} \right)$$


$$F = \frac{d}{dx} \left(\frac{1}{2} CV^2 \right)$$

$$F = \frac{1}{2} V^2 \frac{dC}{dx}$$

$$F = \frac{1}{2} V^2 \left(\frac{\epsilon_0 b}{a} (K-1) \right)$$

$$\boxed{F = \frac{\epsilon_0 b}{2d} (K-1) V^2}$$

constant force

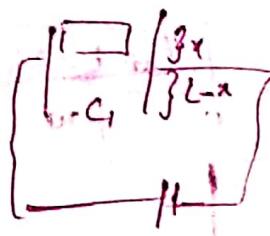

$$F = \frac{\epsilon_0 b}{2d} (k-1) v^2$$

Acceleration of dielectric

$$a = \frac{F}{m}$$

$$a = \frac{\epsilon_0 b}{2md} (k-1) v^2$$

$$s = ut + \frac{1}{2} at^2$$





$$L-x = \frac{1}{2} at^2$$

$$t_0 = \sqrt{\frac{2(L-x)}{a}}$$


Motion of dielectric is oscillating but it is periodic
(Not SHM)

Time period of revolution

$$T = 4t_0 = 4\sqrt{\frac{2(L-x)}{a}}$$

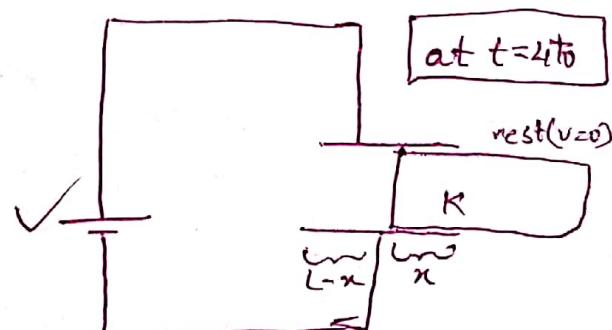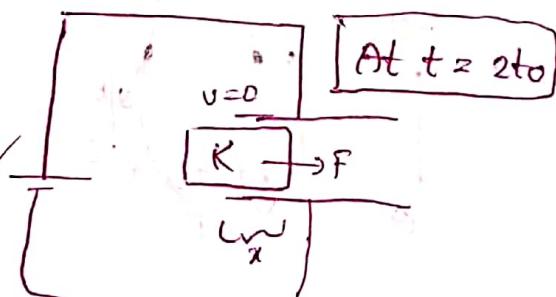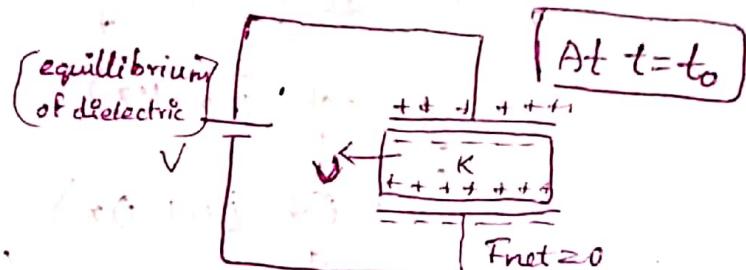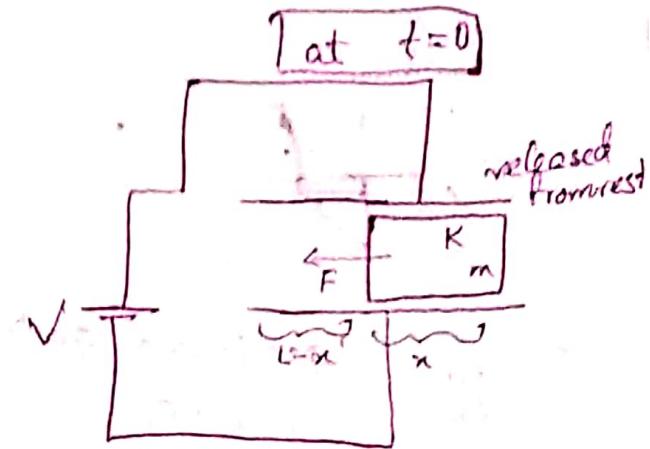

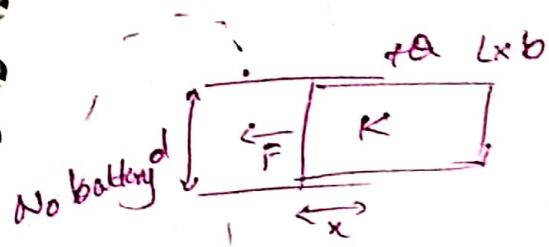Force acting on dielectric if it is not connected to battery



$$F = -\frac{dU}{dx}$$

$$F = \left| \frac{dU}{dx} \right|$$

$$C = C_1 + C_2$$

$$\therefore \frac{\epsilon_0 b}{d} (1 + (K-1)x)$$

$$\frac{dC}{dx} = \frac{\epsilon_0 b}{d} (K-1)$$

$$F = \left| \frac{d}{dx} (U) \right|$$

$$F = \left| \frac{d}{dx} \left(\frac{1}{2} CV^2 \right) \right|$$


$$F = \left| \frac{d}{dx} \left(\frac{C}{2} V^2 \right) \right|$$

$$F = \frac{a^2}{2C} \left(\frac{1}{c^2} \frac{dC}{dx} \right)$$

$$F = \frac{a^2}{2C^2} \left[\frac{\epsilon_0 b}{d} (K-1) \right]$$

For $\frac{1}{C^2}$ is variable

Q)

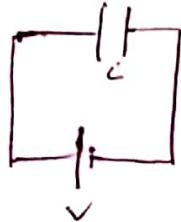

Find the heat produced in the circuit if battery is reverse connected to capacitor



$$Q = C \cdot V = C \cdot V$$

$$Q = 2CV$$

$$W_b = Q \cdot V$$

$$W_b = 2CV^2$$


$$W_b = \Delta V + \text{heat lost}$$

$$\text{heat lost} = W_b - \Delta V$$


$$= 2CV^2 - \left(\frac{1}{2}CV^2 - \frac{1}{2}CV^2 \right)$$

$$\text{heat lost} = 2CV^2$$


a)

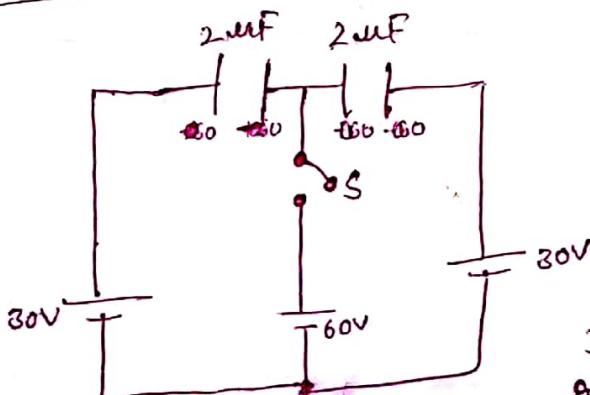

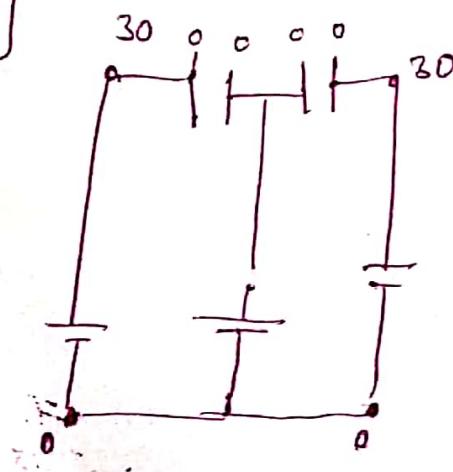Find the heat produced in the circuit if switch is closed.


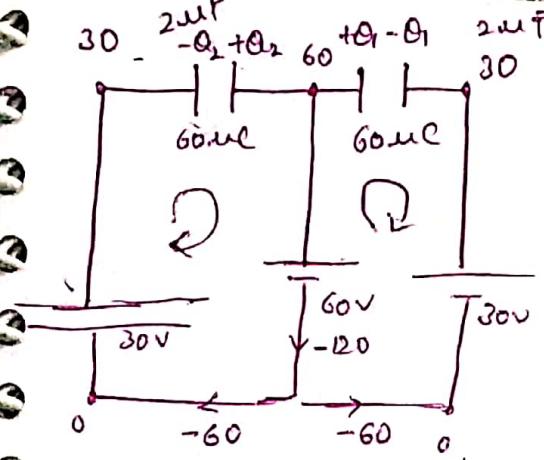
$$Q = \frac{1}{2} \times \frac{1}{2} \times 2 \times 30 \times 30 = 1800$$



$$-\frac{Q_1}{2} - 30 + 60 = 0$$

$$\frac{Q_1}{2} = 30$$

$$Q_1 = 60 \mu C$$

$$\frac{+Q_2 - 60 + 30}{2} = 0$$

$$Q_2 = 60 \mu C$$

$$U_f = \frac{1}{2} \times \frac{1}{2} \times C \times V^2$$

$$\text{Work done by } 60V \text{ battery} = 120 \times 60 = 7200 \mu J = 7.2 \text{ mJ}$$

$$\text{Energy absorbed by the battery of } 30V = 60(30) = 1800 \mu J$$

$$= 1.8 \text{ mJ}$$

$$\text{Energy stored in the capacitor} = \left(\frac{Q^2}{2C}\right) = \frac{60 \times 60}{2 \times 2 \mu F} = \frac{3600}{2} = 1800 \mu J$$


$$= 1.8 \text{ mJ}$$

$$W_b \text{ by } 60V \text{ battery} = \text{energy absorbed by } 30V \text{ battery} + \text{energy stored in capacitor} + \text{Heat lost}$$

$$7.2 = 2(1.8) \text{ mJ} + 1.8 \text{ mJ} + \text{Heat}$$

$$\text{Heat} = 1.8 \text{ mJ}$$

Q) $\frac{F}{2\epsilon_0}$

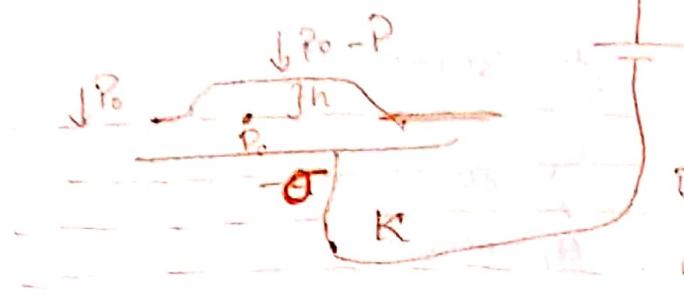


Find the height raised by the dielectric liquid surface.

Dielectric constant - K
density - ρ

$$F = \frac{\sigma^2}{2\epsilon_0} \left(1 - \frac{1}{K}\right)$$

$\rho g h$ =

Concave meniscus - P_0

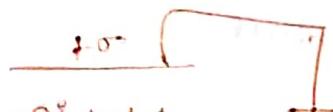

$$P = \frac{F}{A} = \frac{\sigma^2}{2\epsilon_0} \left(1 - \frac{1}{K}\right)$$

$$P = \frac{\sigma^2}{2\epsilon_0} \left(1 - \frac{1}{K}\right) \cdot \frac{h}{\rho g} = \text{atmospheric pressure}$$

Then $\rho g h$ =


$$\text{atmospheric pressure} = P_0 + \rho g h \quad \text{atmospheric pressure} = \text{atmospheric pressure} + \text{pressure due to height}$$

$$P = \rho g h$$

$$\rho g h = \frac{\sigma^2}{2\epsilon_0} \left(1 - \frac{1}{K}\right)$$

$$\Rightarrow h = \frac{\sigma^2}{2\epsilon_0 \rho g} \left(1 - \frac{1}{K}\right)$$

a)

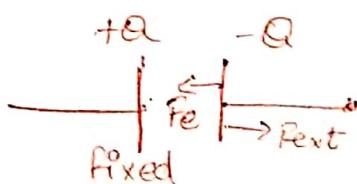

Find the work done by external agent in the moving the plate slowly by $\frac{d}{2}$ distance.

$$W_{ext} = F \times S \theta = \frac{Q^2}{2\epsilon_0} \cdot \frac{d}{2}$$


$$F_e = F_Q$$

$$F_e = F_Q = \frac{\sigma^2}{2\epsilon_0}$$


$$v = 0$$

$$F_{ext} = F_{ext} - \text{restetic force}$$


(a)

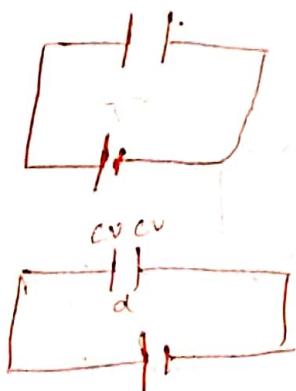

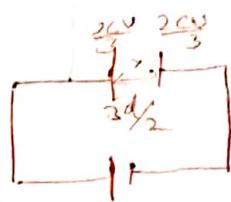Find the work done by external agent in moving the plate slowly by $\frac{d}{2}$ distance



$$\alpha = \frac{\Delta C}{3d}$$

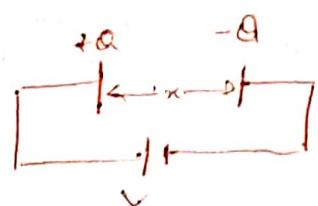

$$C = \frac{\epsilon_0 A}{x}$$

$$\text{charge on capacitor} = \frac{\epsilon_0 A V}{x}$$

$$F = \frac{\epsilon_0 A^2 V}{x^2 2 \epsilon_0 \alpha}$$

$$F = \frac{\epsilon_0 A V}{2 x^2} \Rightarrow dW = F dx = \frac{\epsilon_0 A V^2}{2 x^2} dx$$

$$W_{\text{total}} = \int dW_{\text{ext}}$$

$$= \int_{d/2}^{3d/2} \frac{\epsilon_0 A V^2}{2 x^2} dx$$


$$= \frac{\epsilon_0 A V^2}{2} \left(-\frac{1}{x} \right)_{d/2}^{3d/2}$$

$$= \frac{\epsilon_0 A V^2}{2} \left(-\frac{2}{3d} + \frac{1}{d} \right)$$

$$W_{\text{total}} = \frac{\epsilon_0 A V^2}{6d} = \frac{CV^2}{6}$$

Method ②

$$W_0 + W_{\text{ext}} = \Delta U$$

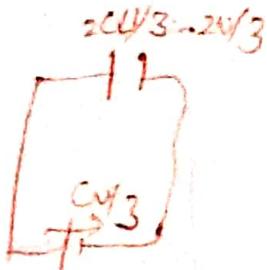


$$-Fv)v + W_{\text{ext}} = \frac{1}{2} \frac{2C}{3} v^2 - \frac{1}{2} C v^2$$


$$-\frac{cv^2}{3} + W_{\text{ext}} = -\frac{1}{6} C v^2$$

$$W_{\text{ext}} = \frac{1}{6} C v^2$$

RC Circuits

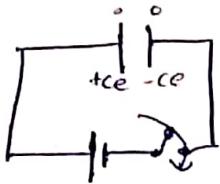


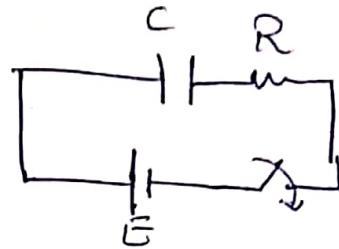Charge on the capacitor increased from 0 to CE in no time
(time taken is zero)



Time will be taken for the capacitor to gain max. charge

\Rightarrow at time t

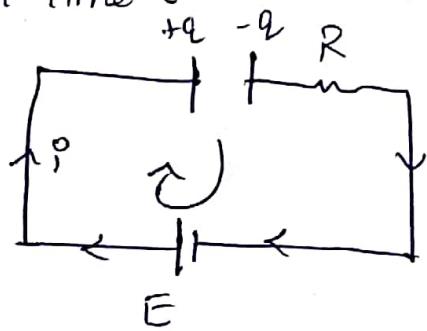

$$\frac{-q}{C} - iR + E = 0$$

$$iR = \frac{-q}{C} + E$$

$$\textcircled{6} \quad \frac{dq}{dt} = -\frac{q}{C} + E$$

$$\frac{CE - q}{C} = \frac{dq}{dt} R$$

$$\int_0^q \frac{dq}{CE - q} = \int_0^t \frac{dt}{RC}$$

$$[-\ln(CE - q)]_0^q = \frac{et}{RC}$$

$$\textcircled{7} \quad \ln\left(\frac{CE - q}{CE}\right) = \frac{-t}{RC}$$

$$1 - \frac{q}{CE} = e^{-t/RC}$$

★
$$q = CE(1 - e^{-t/RC})$$

$$\frac{q}{CE} = 1 - e^{-t/RC}$$

$$q = q_{\max}(1 - e^{-t/RC})$$

$$\text{at } t = \infty, q = CE(1 - e^{-\infty})$$

$$q = CE$$




* Find the current in the circuit.

$$\therefore \frac{dq}{dt} = CR \cdot e^{-t/RC}$$

$$i = \frac{q}{C} e^{-t/RC}$$

$$\Rightarrow i = i_{\max} e^{-t/RC}$$

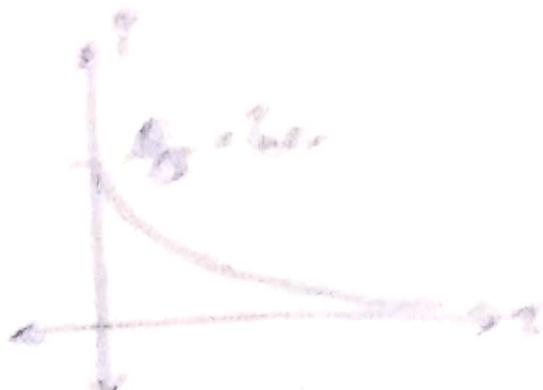

\Rightarrow voltage across the capacitor (P.D)


$$V_C = \frac{Q}{C}$$

$$V_C = \frac{CE(1 - e^{-t/RC})}{C} \Rightarrow V_C = E(1 - e^{-t/RC})$$

\Rightarrow Voltage across the resistor is $V_R = IR$.

$$V_R = i_{\max} e^{-t/RC} \cdot R$$

$$V_R = E e^{-t/RC}$$

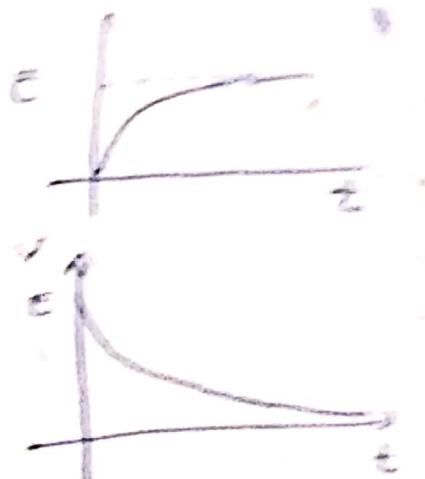


Notes-

* at $t = 0$ (just after switch is closed)

$$Q = 0 \quad i_{\max} = E/R$$

$$V_C = 0 \quad V_R = E$$

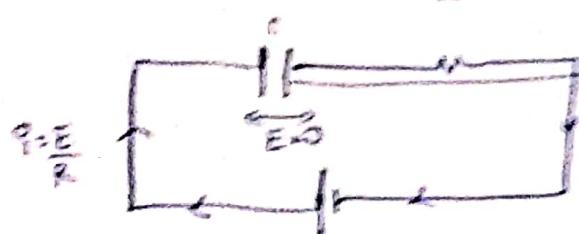

→ capacitor acts as a conducting wire.
(capacitor can be removed)


* at $t = \infty$ (after long time switch is closed)
(steady state)

$$q = CE$$

$$i = 0$$

$$V_C = E$$

$$V_R = 0$$


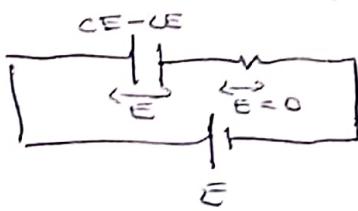


Capacitor acts as insulator as complete charge is filled

* Current in the branch of capacitor is zero.

a) Find the current supplied by the battery at $t = 0$ and $t = \infty$

at $t = 0$

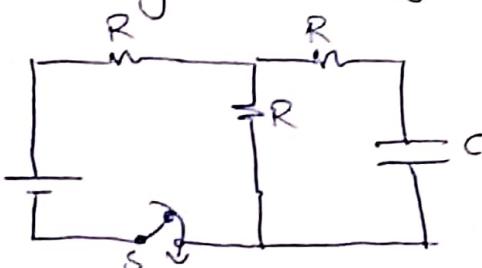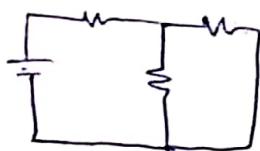


$$R_{\text{eff}} = 3R/2$$

$$E = i R_{\text{eff}}$$

$$i = \frac{2E}{3R}$$

at $t = \infty$

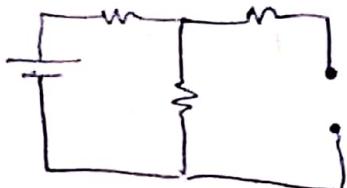

$$R_{\text{eff}} = 2R$$


$$E = i(2R)$$

$$i = \frac{E}{2R}$$

Time t
 $q = q_{\max} (1 - e^{-t/T})$

at time t the current achieves 63%

$$E = R_{\text{eff}}$$

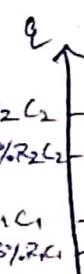

the total

Time constant (T)

$$q = q_{\max} (1 - e^{-t/RC})$$

at $t = RC$




$$q = q_{\max} \left(1 - \frac{1}{e}\right)$$

$$q = q_{\max} \left(1 - \frac{1}{2.7}\right)$$

i.e Time constant is the time at which a capacitor achieves 63% of its maximum achievable charge

$$\boxed{\cancel{T = RC}}$$

$$\boxed{T = RC}$$

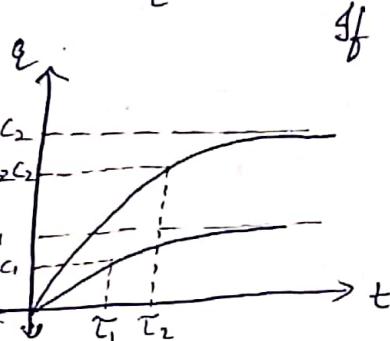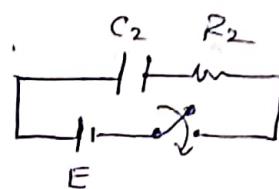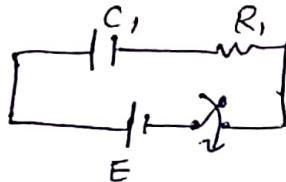

if $R_1C_1 < R_2C_2$

a)

if switch is closed at $t=0$, find the total heat generated (or) lost through resistor.

$$i = \frac{E}{R} e^{-t/RC}$$

$$H = \int i^2 R dt$$


$$= \frac{E^2}{R} \int e^{-2t/RC} dt$$

$$= \frac{RCE}{R^2} \left[\frac{e^{-2t/RC}}{-1} \right]_0^\infty$$

$$= \frac{RCE^2}{2R} \left[0 + 1 \right] = \frac{RCE^2}{R^2} = \frac{CE^2}{2}$$

Work done by battery = $(CE) E = CE^2$

a)

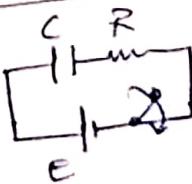

If the switch is closed, find the max rate of energy stored in capacitor

$$\text{Energy in capacitor} = \frac{1}{2} CU^2 = \frac{Q^2}{2C}$$

$$= (CE)^2 (1 - e^{-t/RC})^2$$

$$U = \frac{1}{2} CE^2 (1 - e^{-t/RC})^2$$

$$\left\{ \frac{dU}{dt} = \frac{E^2}{R} (1 - e^{-t/RC}) e^{-t/RC} \right\}$$

$$\frac{dU}{dt} = \frac{1}{2} CE^2 2(1 - e^{-t/RC}) \frac{e^{-t/RC}}{RC} = 0$$

$\therefore f(x) = (1-x)x^2$ will be

$$\frac{dU}{dt} = \frac{E^2}{R} (e^{-4RC} - e^{-2t/RC}) \quad \text{max at } x = \frac{1}{2}$$

$$\frac{d^2U}{dt^2} = \frac{E^2}{R} \left(\frac{-e^{-t/RC}}{RC} + \frac{2e^{-2t/RC}}{RC} \right)$$


$$= \frac{E^2}{R^2 C} (2e^{-2t/RC} - e^{-t/RC}) = 0$$

$$\left(\frac{dU}{dt} \right)_{\text{max}} = \frac{E^2}{R} \left(1 - \frac{1}{2} \right) \frac{1}{2}$$


$$2e^{-2t/RC} = e^{-t/RC}$$

$$e^{-t/RC} = \frac{1}{2}$$
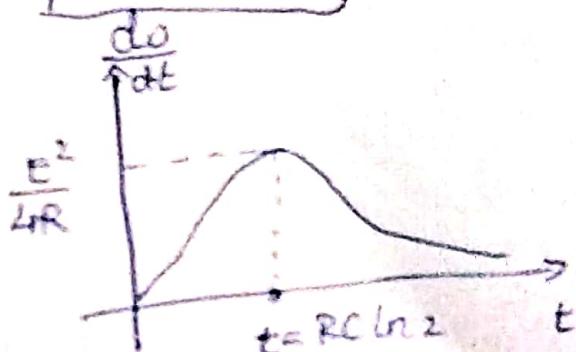
$$\left(\frac{dU}{dt} \right)_{\text{max}} = \frac{E^2}{4R}$$



a)

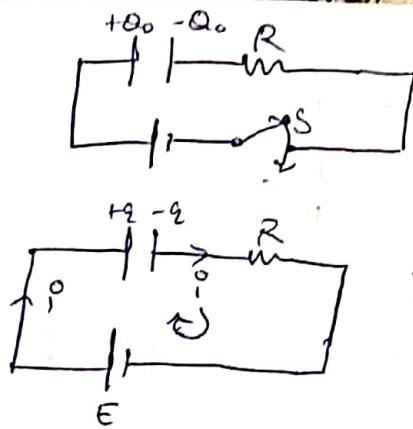

If switch is closed at $t=0$,
find the charge on the capacitor
as a function of time.

$$\frac{-Q}{C} - iR \cdot E = 0$$

$$\frac{CE-Q}{C} = \frac{dQ}{dt} R$$

$$\int \frac{dQ}{CE-Q} = \int \frac{dt}{RC}$$




$$\left[\frac{\ln(CE-Q)}{-1} \right]_{Q_0}^Q = \frac{t}{RC}$$

$$\ln \left(\frac{CE-Q}{CE-Q_0} \right) = \frac{t}{RC}$$


$$CE-Q = (CE-Q_0)e^{-t/RC}$$

$$Q = CE - (CE-Q_0)e^{-t/RC}$$


$$Q = CE - (CE-Q_0)e^{-t/RC}$$

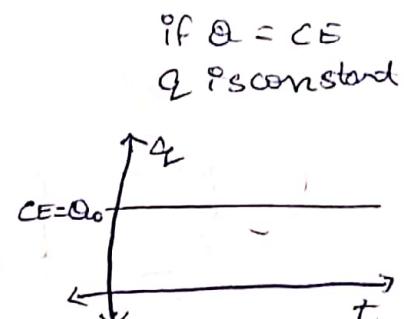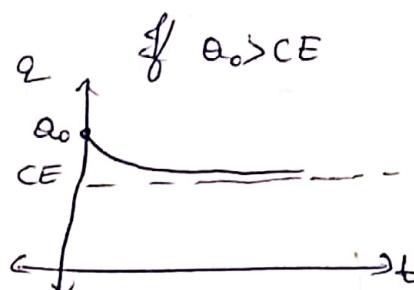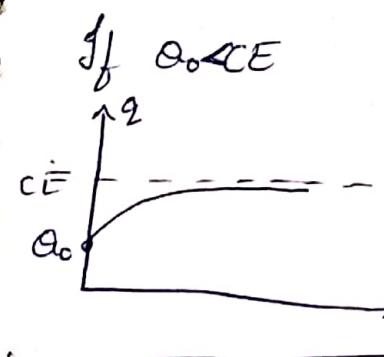

Note

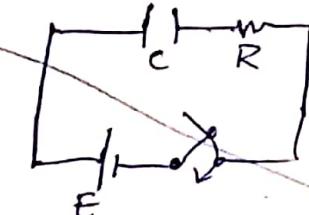Time constant = $\tau = RC$

$$Q = Q_{\max} (1 - e^{-t/RC})$$

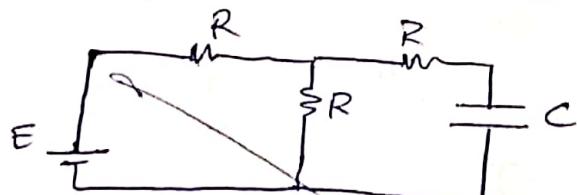


Time constant of circuit

(1) short circuit the battery



$$R_{\text{net}} = \frac{3R}{2}$$

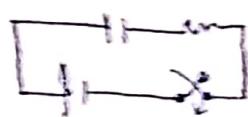
(2) Open the capacitor $\tau = \frac{RC}{2}$ (3) Find R_{net} across capacitor terminals(4) $I = CR_{\text{net}}$



$$\text{Time constant} = \tau = RC$$

$$Q = Q_{\max} (1 - e^{-t/\tau})$$

$$Q = Q_{\max} (1 - e^{-t/RC})$$

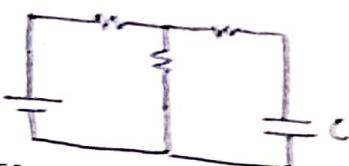

Time constant of circuit

(1) short circuit the battery

(2) Open the capacitor

(3) Find the Root across the capacitor terminal

$$(4) \tau = CR_{\text{root}}$$


$$Q = Q_{\max} (1 - e^{-t/\tau}) = Q_{\max} (1 - e^{-t/CR_{\text{root}}})$$



$$R_{\text{root}} = \frac{3R}{2}$$

$$\tau = \frac{CR}{2}$$

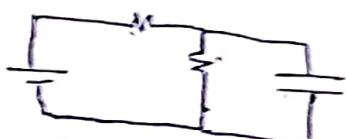For finding Q_{\max} on capacitor i.e. at $t = \infty$




$$\therefore Q_{\max} = \frac{CE}{2}$$

$$Q = \frac{CE}{2} \left(1 - e^{-\frac{2t}{RC}} \right)$$

Finding max charge on capacitor

a)

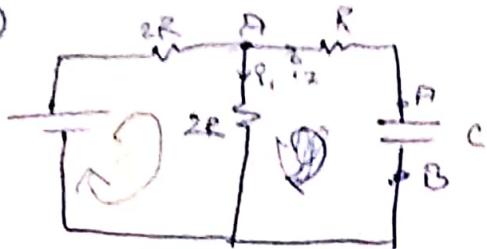

$$-i_1 \times 2R + E - i_1 2R - i_2 2R = 0$$

$$E = i_1 4R + i_2 2R$$

$$\frac{R_{\text{ext}}}{R_B} = 2R$$

$$q = q_{\max} (1 - e^{-t/2RC})$$

$$i_2 = R_B i_{\max} (e^{-t/2RC})$$

$$i_2 = \frac{E}{4R} (e^{-t/2RC})$$

$$i_1 = \frac{E}{4R} + \frac{i_2}{2}$$


$$= \frac{E}{4R} + \frac{E}{8R} (e^{-t/2RC})$$

$$i_1 = \frac{E}{8R} (2 + e^{-t/2RC})$$

$$Q_0 = CE$$

[Ans]

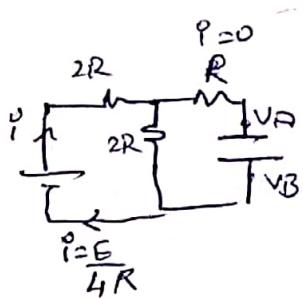charge on capacitor $q_t = q_{\max} (1 - e^{-t/2RC})$



$$i_2 = \frac{dq}{dt} = \frac{CE}{2} \left(-\left(\frac{1}{2RC}\right) e^{-t/2RC} \right)$$

$$i_2 = \frac{E}{4R} e^{-t/2RC}$$

$$-i_1 R - \frac{q}{C} + i_2 (2R) = 0$$

$$i_2 (2R) = i_1 R + \frac{q}{C}$$


$$i_2 (2R) = \frac{E}{4R} e^{-t/2RC} + \frac{E}{2} (1 - e^{-t/2RC})$$

$$i_2 = \frac{E}{8R} (2 - e^{-t/2RC})$$


Current from battery $i = i_1 + i_2$

$$= \frac{E}{4R} e^{-t/2RC} + \frac{E}{8R} (2 - e^{-t/2RC}) = \frac{E (2 + e^{-t/2RC})}{8R}$$



Q) Discharging of capacitor

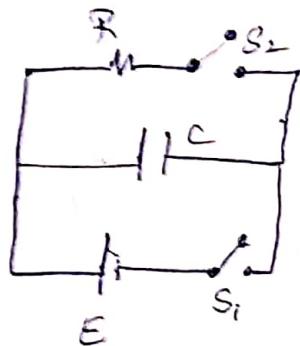


If S_1 is closed and S_2 is open

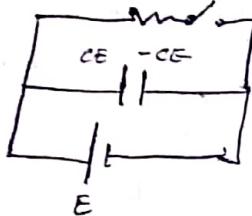

If S_2 is closed and S_1 is open

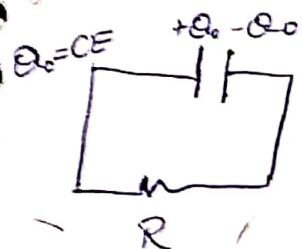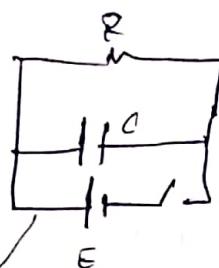

at $t = 0$


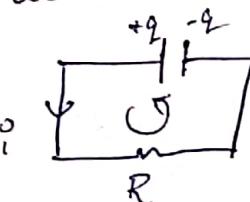


$$-iR + \frac{Q}{C} = 0$$

$$\frac{Q}{C} = iR$$

$$\frac{Q}{C} = -\frac{dQ}{dt} R$$
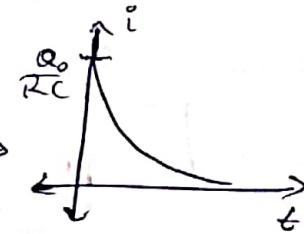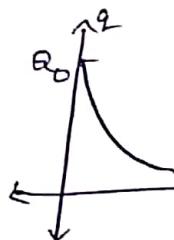
$$\int \frac{dQ}{Q} = \int -\frac{dt}{RC}$$




$$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC} \leftarrow \left(\ln\frac{Q}{Q_0}\right)^t = \frac{-t}{RC} \leftarrow$$

$$Q = Q_0 e^{-t/RC}$$

$$i = \frac{dQ}{dt} \Rightarrow i = \frac{Q_0}{RC} e^{-t/RC}$$

Q)

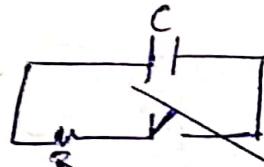

$$dH = i^2 R dt$$

$$\int dH = \int \frac{Q_0}{RC} R e^{-t/RC} dt$$

$$= \left[-\frac{Q_0}{C} \cdot e^{-t/RC} \cdot R \right]$$

$$H = Q_0 R e^{-t/RC} - Q_0 R$$

$$H = Q_0 R (e^{-t/RC} - 1)$$

Q)



Find the heat lost through resistor.

$$\text{current} = i = \frac{Q}{RC} e^{-t/RC}$$

~~$$H = \int i^2 R dt$$~~

$$H = \int \frac{Q^2 R}{R^2 C^2} e^{-2t/RC} dt$$

$$H = \frac{Q^2}{RC^2} \int_0^\infty e^{-2t/RC} dt$$

$$H = \frac{Q^2}{RC^2} \left(\frac{e^{-2t/RC}}{-2/RC} \right)_0^\infty$$

$$= \frac{Q^2}{RC^2} \left(\frac{RC}{2} \right) (e^{-\infty} - e^0)$$

$$H = -\frac{Q_0^2}{2C} (0 - 1)$$

$$H = \frac{Q_0^2}{2C}$$

Energy stored in capacitor would be lost through resistor in discharging circuit
Heat lost = change in energy of capacitor

$$= \frac{Q_0^2}{2C} - 0$$

$$= \frac{Q_0^2}{2C}$$